

## **Mini Project (Design and Implementation in Logisim and HDL)**

### **Parking Management System**

#### **Team Members:**

1. Konatham Naga Mukesh  
221CS132  
konathamnagamukesh.221cs132@nitk.edu.in  
8639550996
2. Lakkimsetti Sreyas  
221CS134  
mrlakkimsettisreyas.221cs134@nitk.edu.in  
9611275188
3. Tanay Praveen Shekokar  
221CS159  
tanayshekokar.221cs159@nitk.edu.in  
7022420056

#### **Abstract:**

With the growing issues of urbanisation and limited parking resources, the development of a user-friendly Parking Management System is critical. This project provides a comprehensive system that combines parking slot occupancy detection and real-time slot availability display, with the user experience and parking facility efficiency as the top priorities.

The goal behind this method is to address frequent urban difficulties such as traffic congestion and long parking search periods, which cause annoyance among vehicle owners. By utilising modern occupancy sensors, central control units, and digital displays, we hope to simplify the parking experience. It detects car presence reliably, updates real-time slot availability, and communicates this information to users, minimising the time and effort required to find a parking spot.


Our unique contribution is the seamless integration of these components, which improves customer pleasure while optimising space utilisation. The system keeps track of entry and exit times, which can be utilised for security and auditing. Furthermore, the obtained data can be used to guide future improvements and data-driven decision-making.

Our Parking Management System, by focusing on improving user experience and facility management, provides a realistic answer to the issues faced by urban parking, ultimately leading to more efficient and user-centric urban transportation solutions.
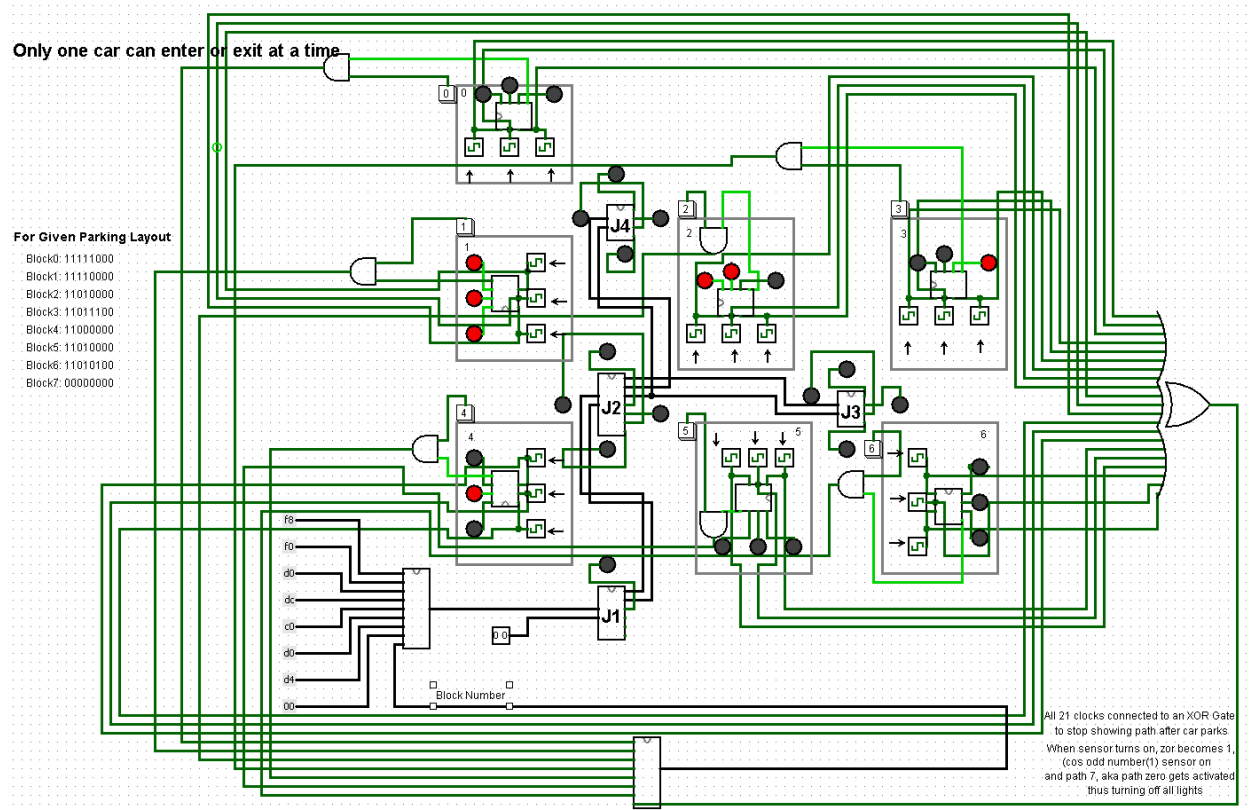
## Brief Description

(Simulation to describe the user interaction, i.e. Output for various inputs)

Let us say this is how the screen looks originally



Each Block has a button labelled 0,1,2.... Depending on block number

Over here, each block has 3 LEDs


If the LED is switched on, it means that particular parking slot in that block is filled

Looking at this diagram, the user can choose which block he wants to park in


NOTE: Junction1 is the entrance

Let us say, the user wants to park in block2

He presses the button for block2

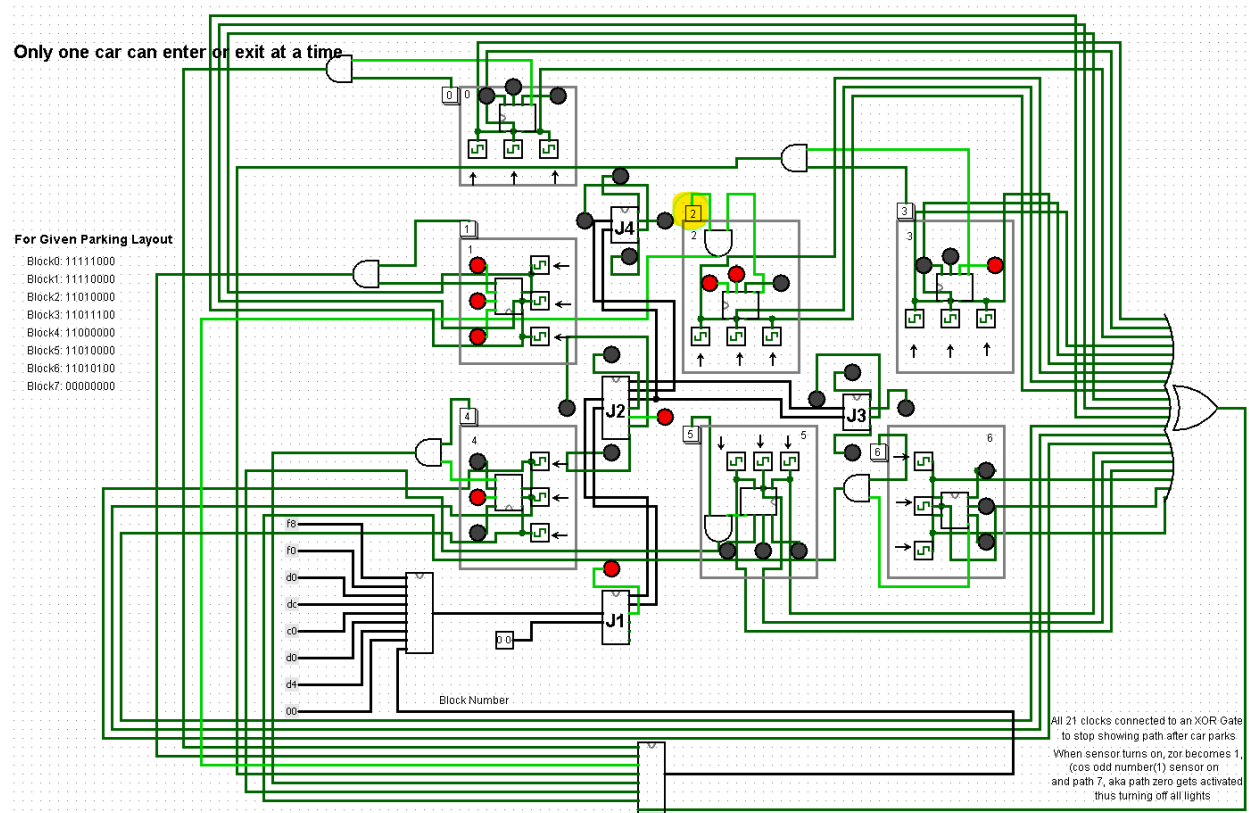

and releases it

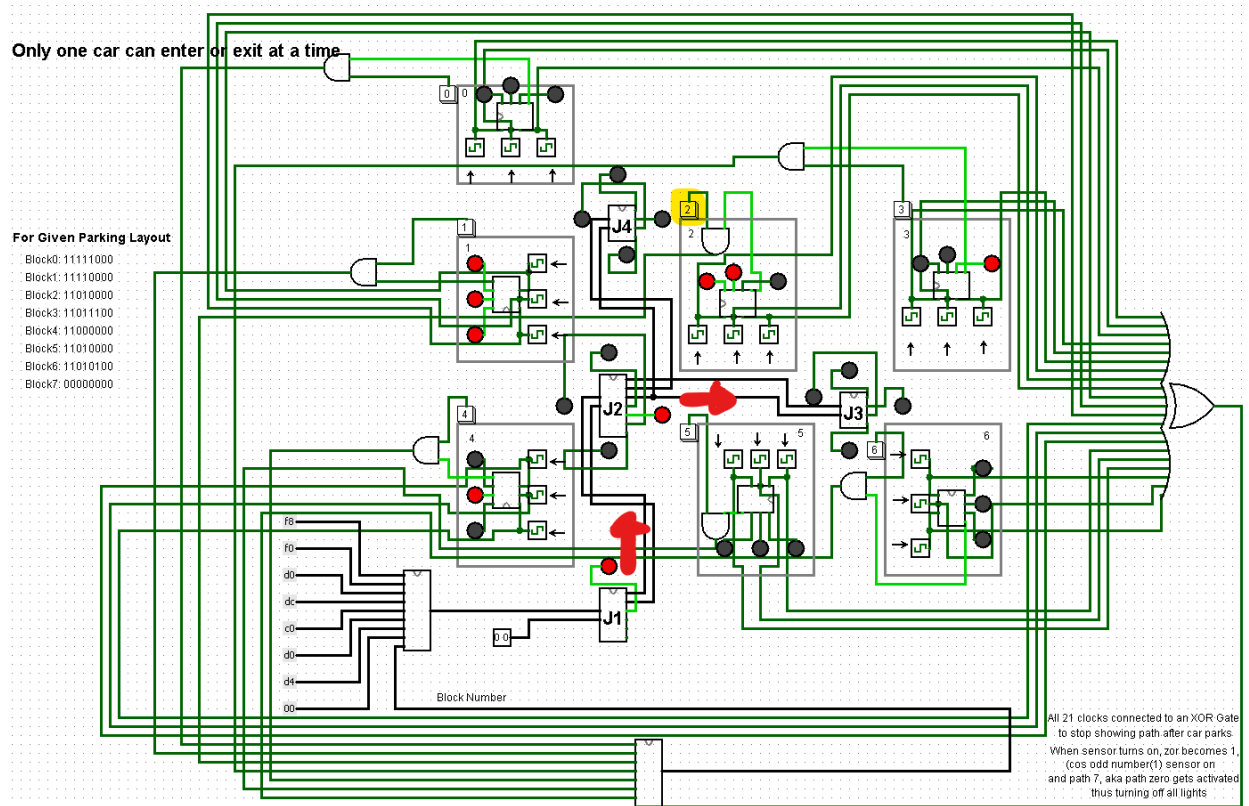

**NOTE: Junction1 is the entrance**

Now, as we can see, the path to Junction2 is generated

At junction1, the north led is on, which means at junction1, the user must go straight


At junction2, the west led is on, which means at junction2, the user must go right

If the user follows the above instructions, he will reach the road from which he can enter the parking slot

Now, when the user enters the 3rd slot at block2

The third sensor(clock), which is present at the entrance of the slot turns on

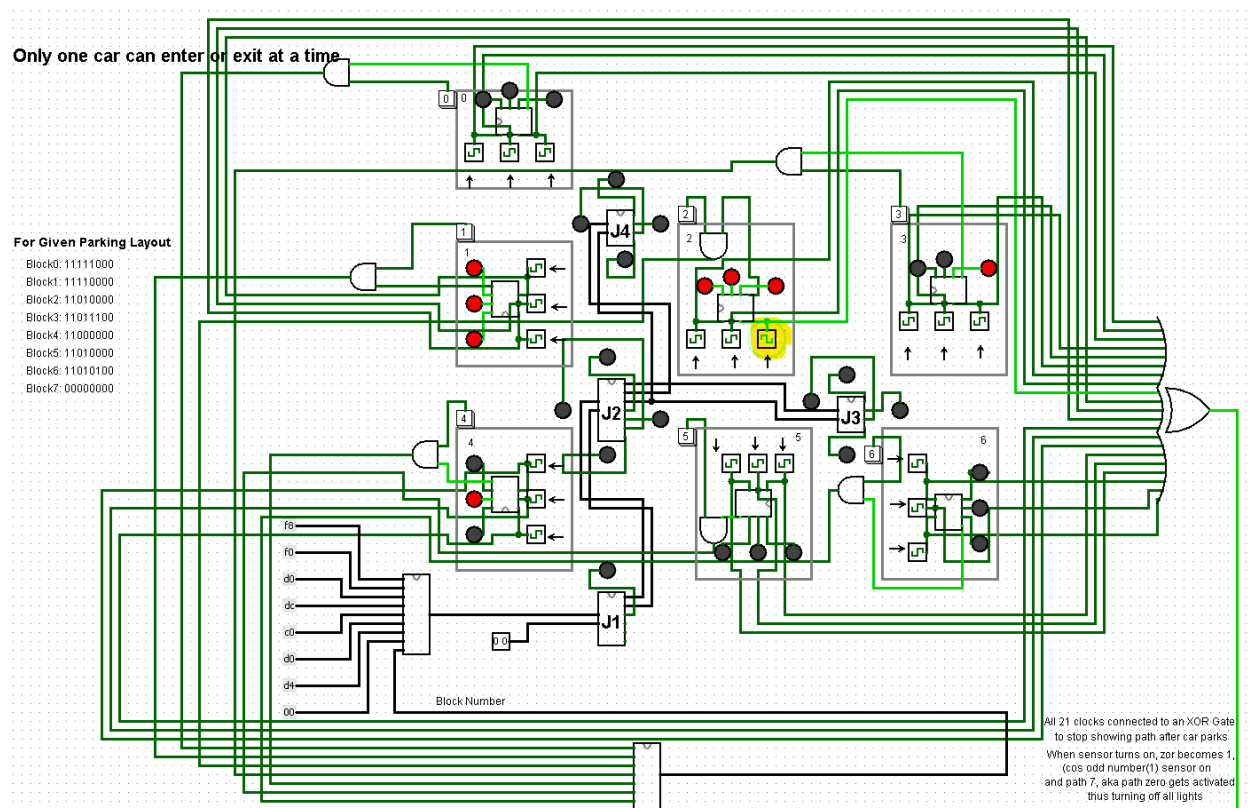Which means, the person is going to enter in that slot




Now that this clock is turned on, the path towards block2 disappears

Bcos the car will be parked in this slot now, and thus doesnt need the directions anymore

Once the car parks in that slot

He will cross the entrance of that slot

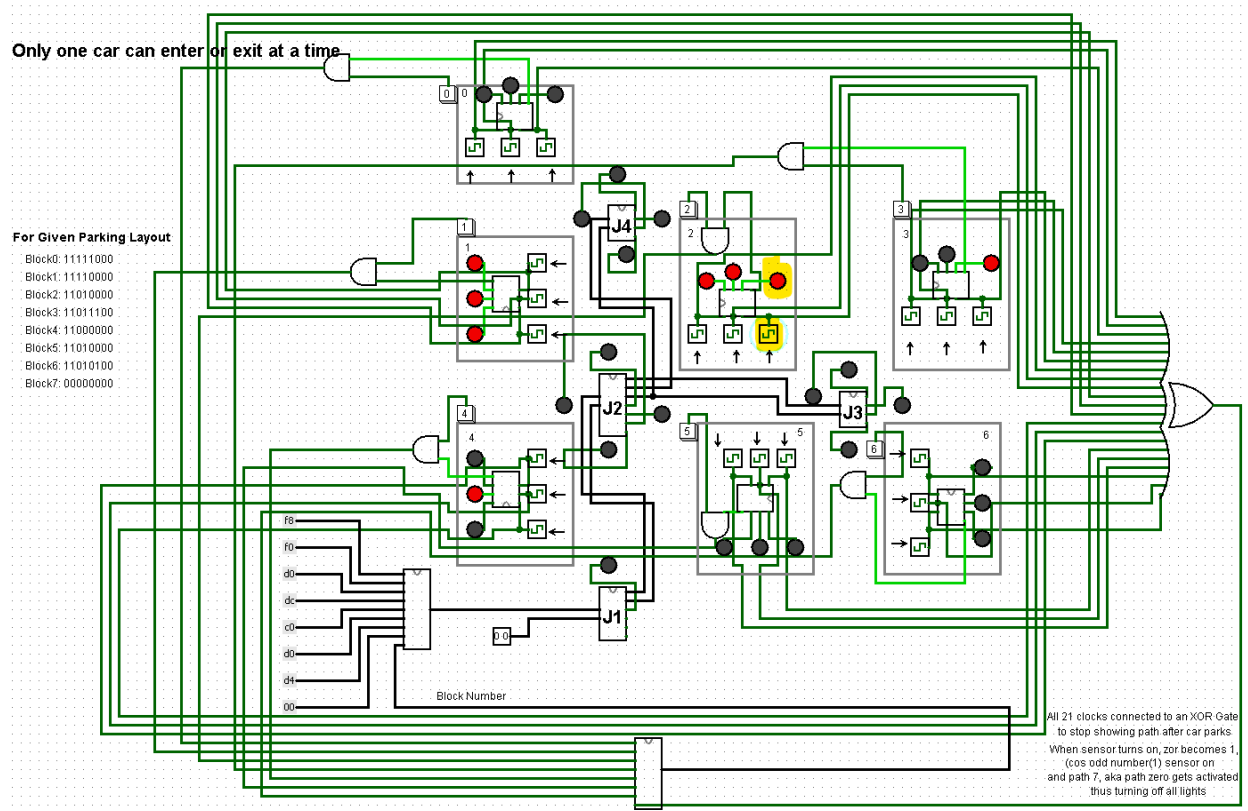Thus, the sensor(clock) for that slot becomes 0 again




As we can see,


Now, on the screen we can see that the third slot of block 2 which was previously empty is now full as displayed by the LED after the current user parked in that slot

Now, let us see what happens in the case of the next user

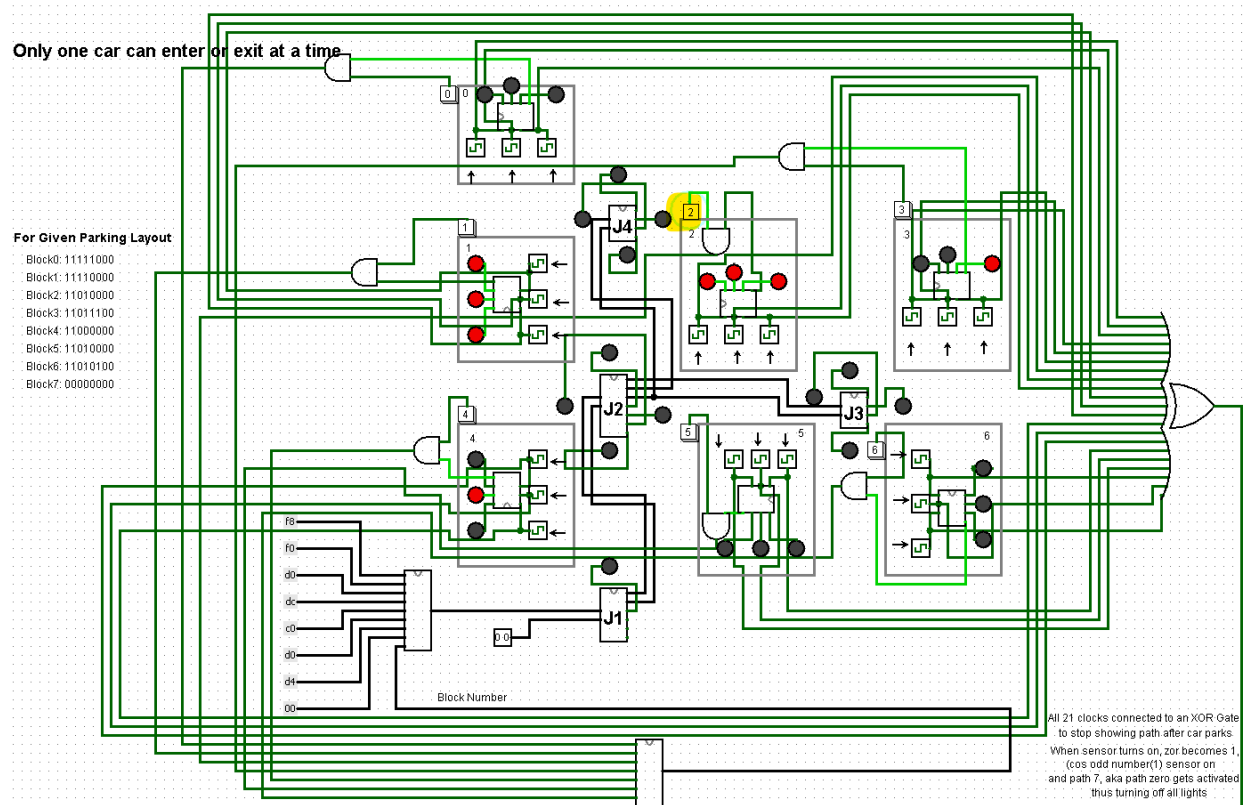Let us say, the user presses the block2 button and releases it




And releases it

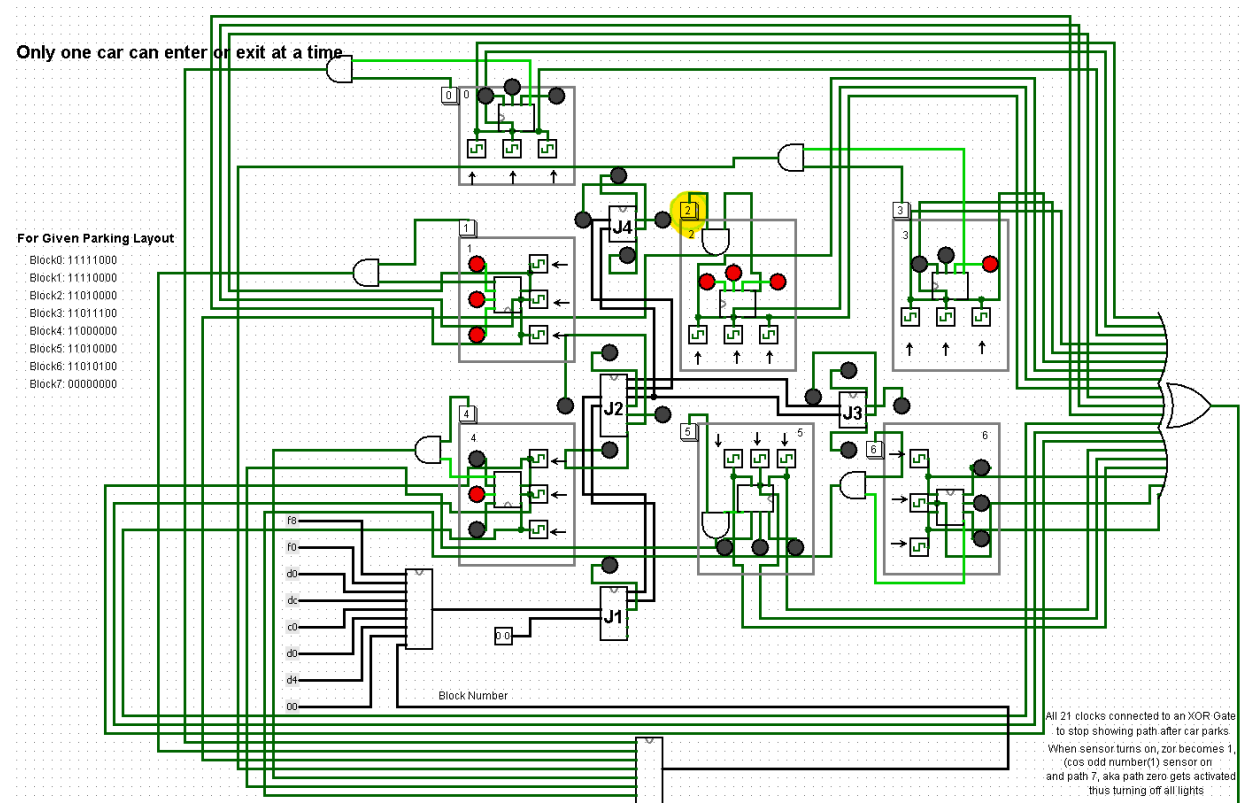

even though there are no vacant parking slots

No path to that block will be shown bcos, that block has no vacant slots

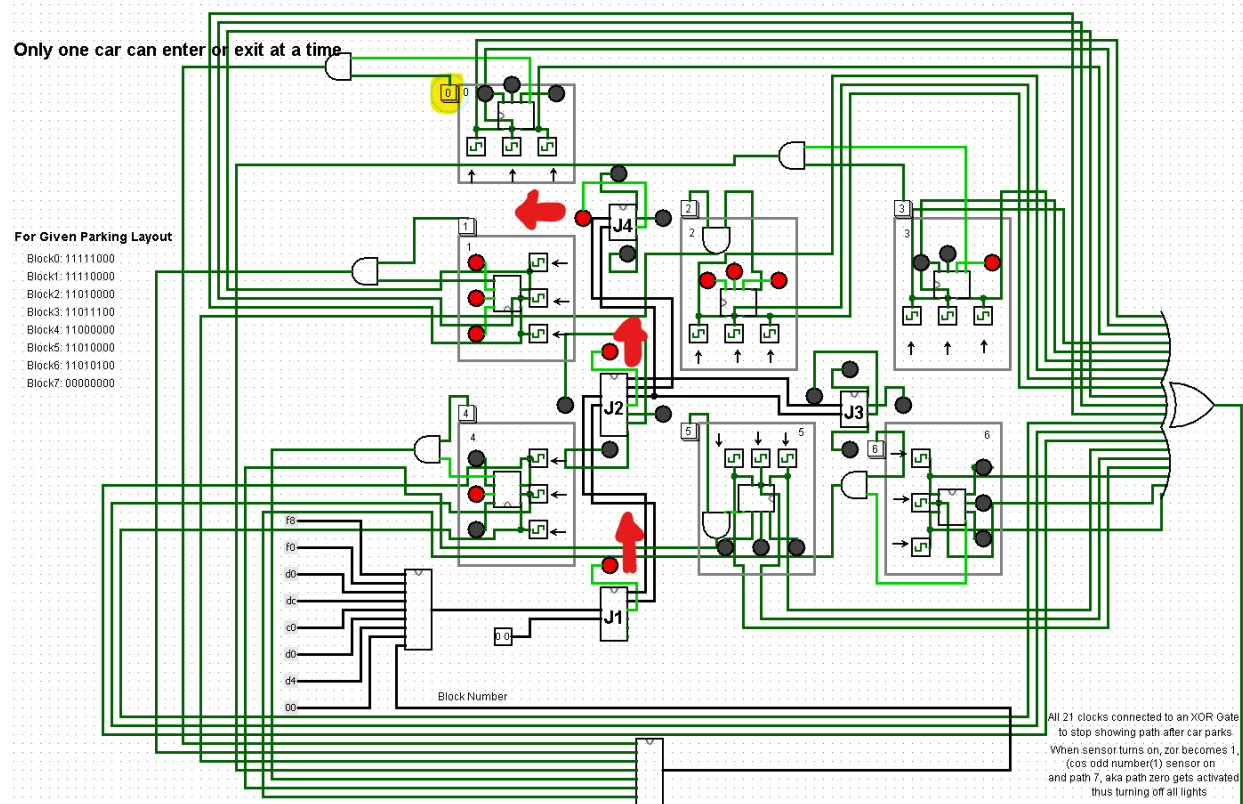
So, the user must select another block  
 Let us assume the user chooses block 0 now  
 He presses and releases the button for block 0



Now, the path for junction 0 is displayed as we can see from the code  
 Go straight from junction1  
 Go straight at junction2  
 Take a left at junction3

But, let us say, the user doesnt follow the path and goes to block 6  
 And parks in the first slot

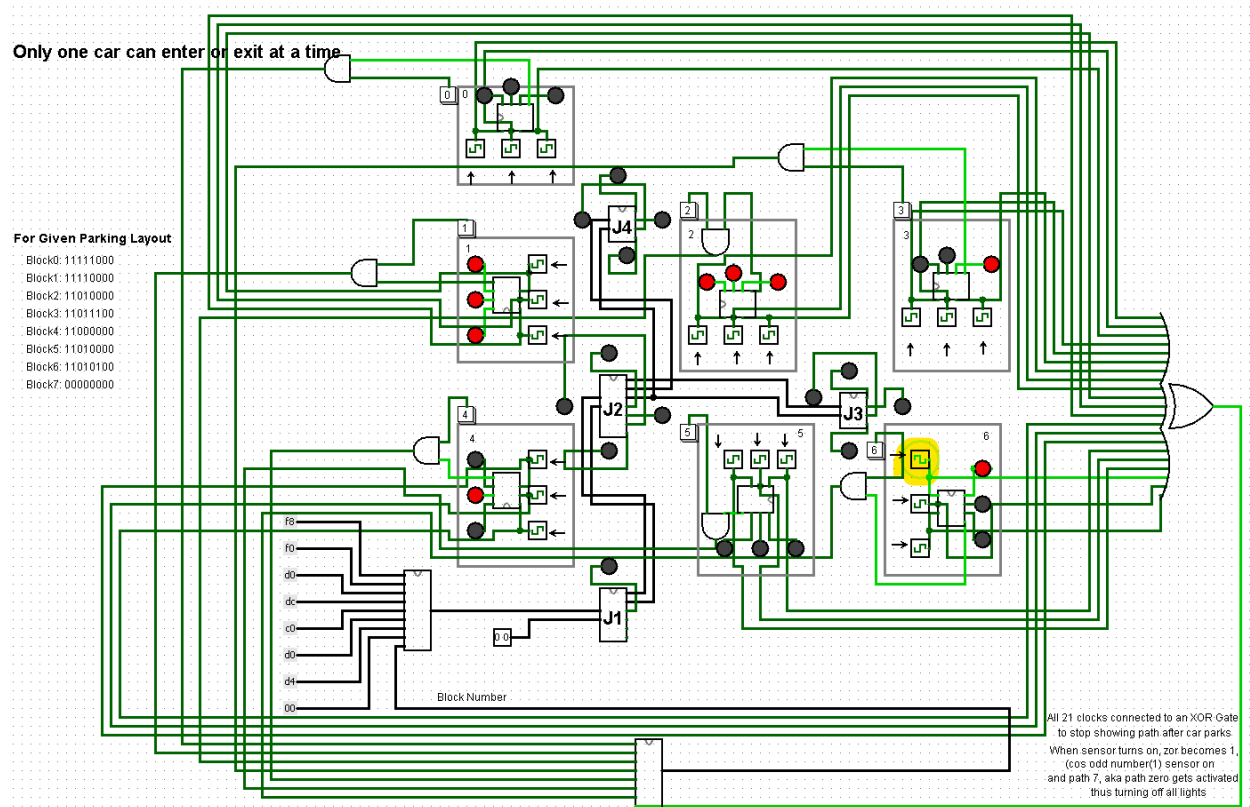
Now, when the user enters the 1st slot at block6  
 The first sensor(clock), which is present at the entrance of the slot turns on  
 Which means, the person is going to enter in that slot



Now that this clock is turned on, the path towards block0 disappears  
Bcos the car will be parked in this slot now, and thus doesnt need the directions anymore

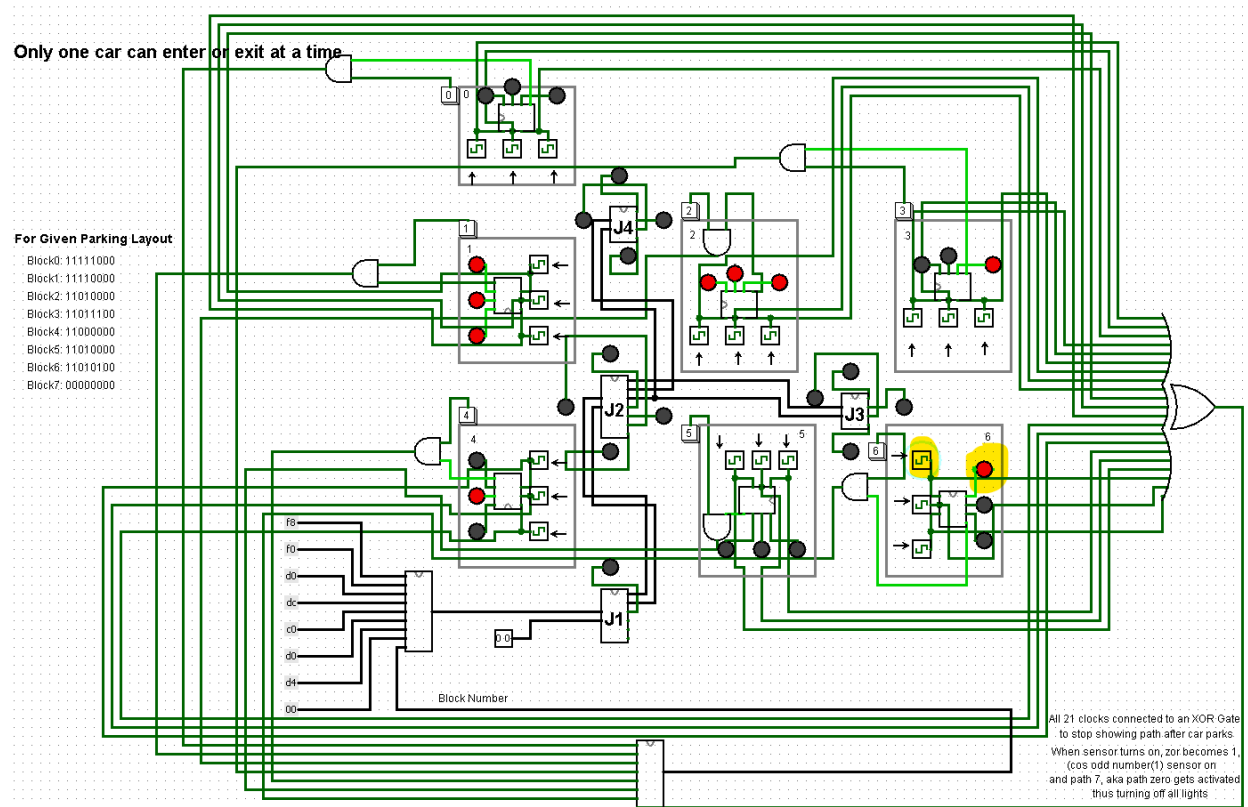Once the car parks in that slot  
He will cross the entrance of that slot  
Thus, the sensor(clock) for that slot becomes 0 again





As we can see,

Now, on the screen we can see that the first slot of block 6 which was previously empty is now full as displayed by the LED after the current user parked in that slot

Now let us say, the car in the 2nd slot from block 1 is leaving


Bcos, the car is leaving, it passes through the entrance of that slot

So that sensor(clock) becomes 1

Only one car can enter or exit at a time

For Given Parking Layout

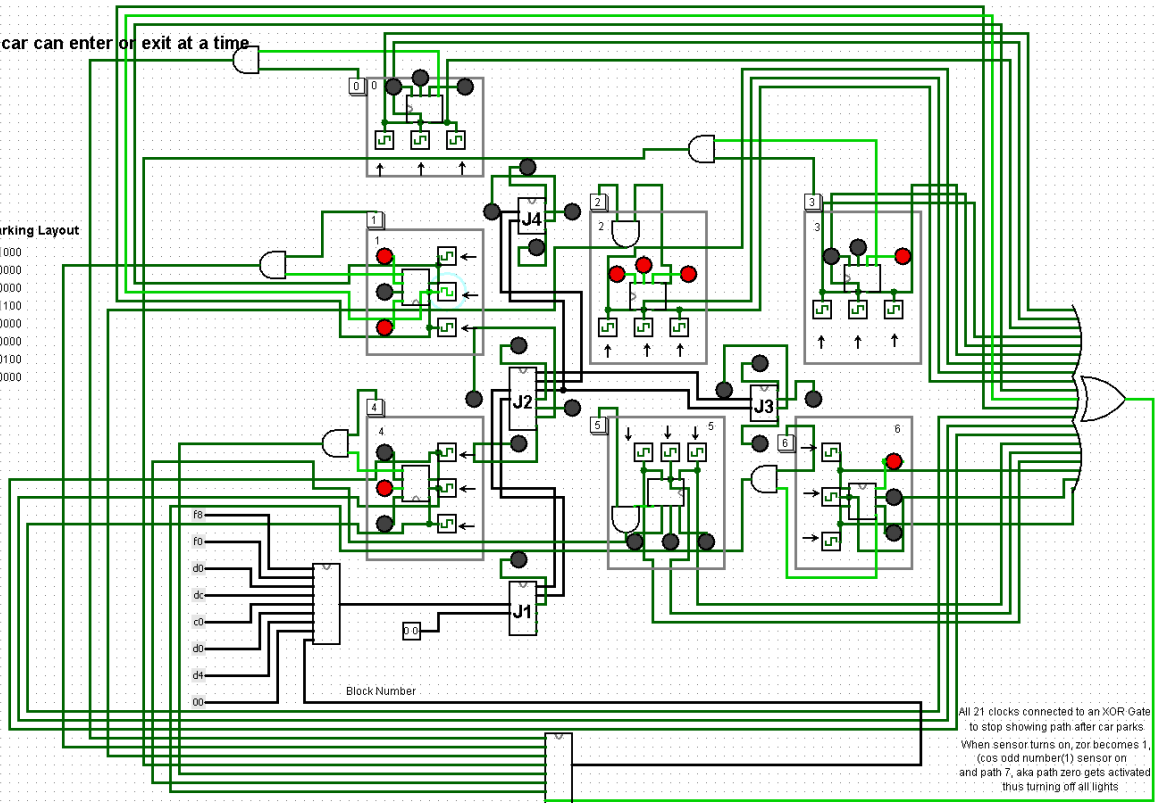Block0: 11111000  
Block1: 11110000  
Block2: 11010000  
Block3: 11011100  
Block4: 11000000  
Block5: 11010000  
Block6: 11010100  
Block7: 00000000




All 21 clocks connected to an XOR Gate to stop showing path after car parks. When sensor turns on, xor becomes 1, (cos odd number(1) sensor on and path 7, aka path zero gets activated thus turning off all lights

Now when he leaves that slot,  
The clock sensor becomes 0 again

Only one car can enter or exit at a time

For Given Parking Layout

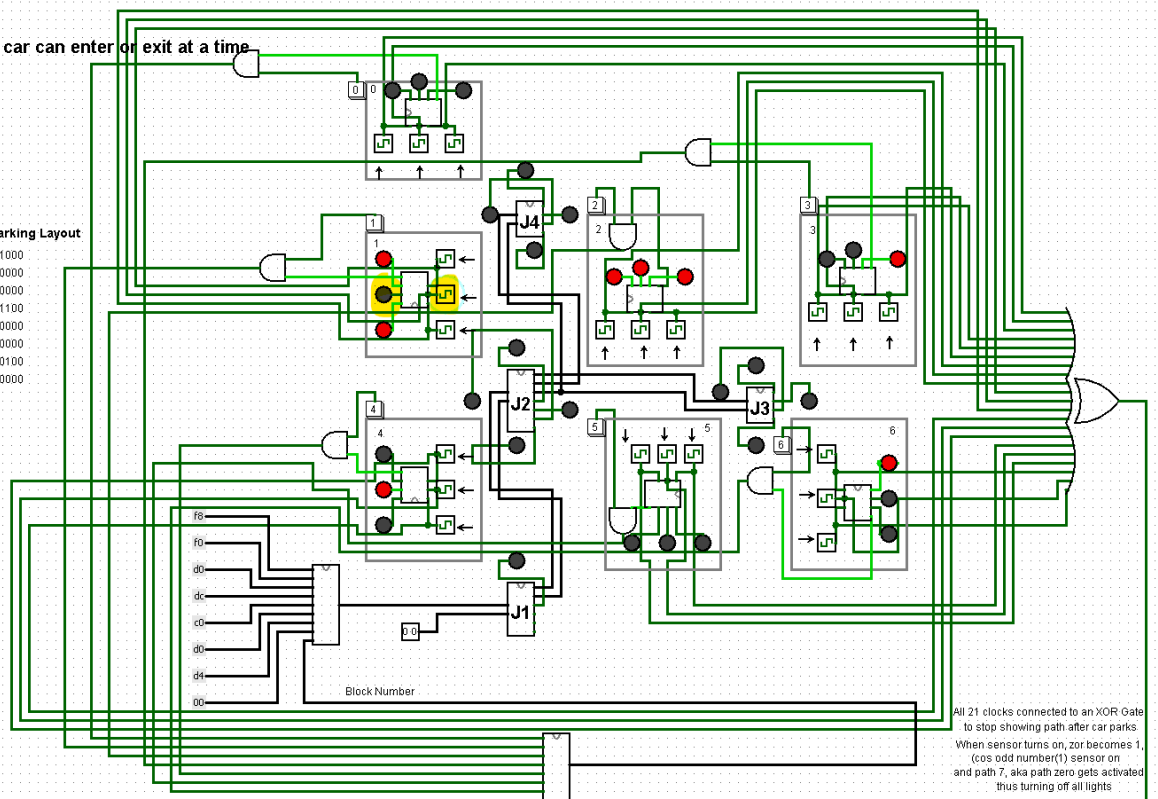Block0: 11111000  
Block1: 11110000  
Block2: 11010000  
Block3: 11011100  
Block4: 11000000  
Block5: 11010000  
Block6: 11010100  
Block7: 00000000




All 21 clocks connected to an XOR Gate to stop showing path after car parks. When sensor turns on, xor becomes 1, (cos odd number(1) sensor on and path 7, aka path zero gets activated thus turning off all lights

As we can see,

The 2nd slot of block1, which was previously filled is now empty  
Thus, there is a vacant spot available in block1 now

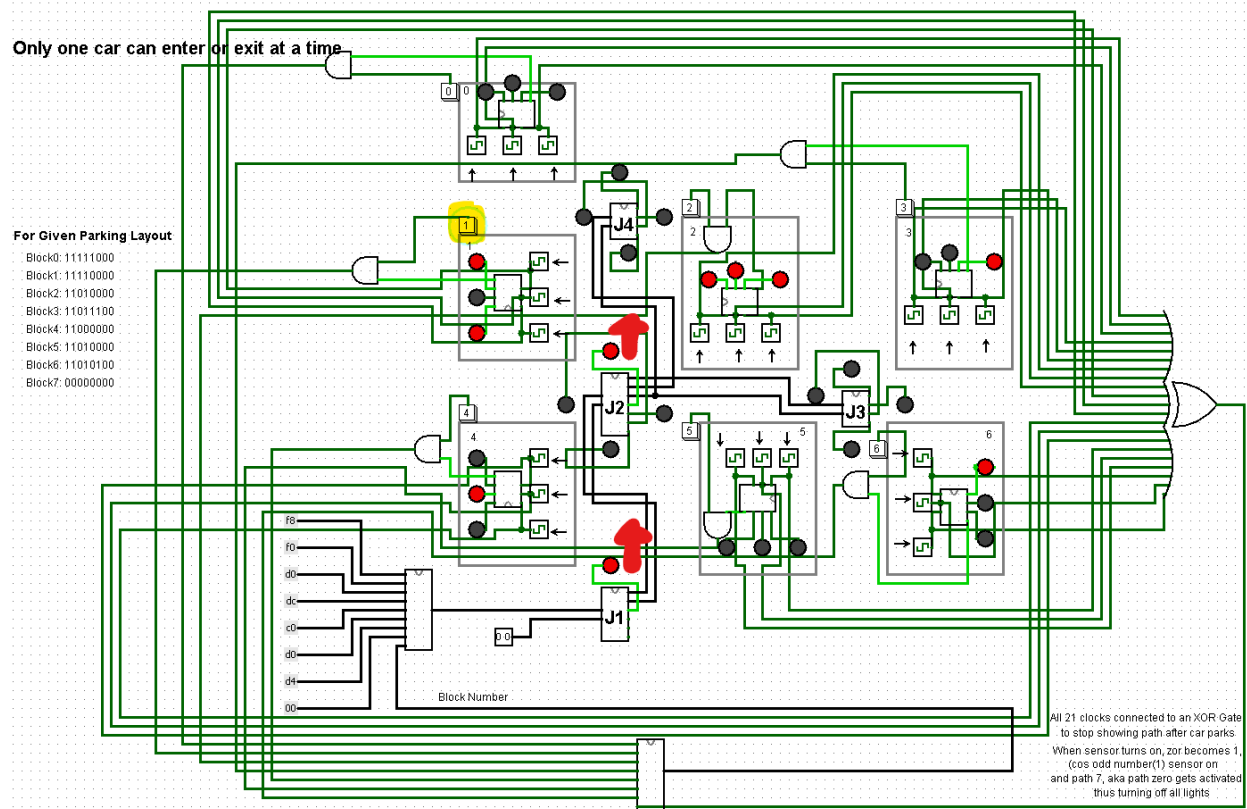So, if the next user presses the block1 button, the path to block1 will be displayed



The aforementioned scenario seamlessly amalgamates all potential possibilities and eloquently articulates the ensuing outcomes therewithin.


And this thus, explains what the project does  
We will soon explain the working in the next section

## Working:


Let us go in a sequential order, starting from pressing a button until parking in a slot  
Where the working will be explained step by step,  
and each component will be explained on its first occurrence based on the above order

The user starts by pressing a button for a particular block  
The way a button works it  
When it is pressed, it is considered that the input is 1

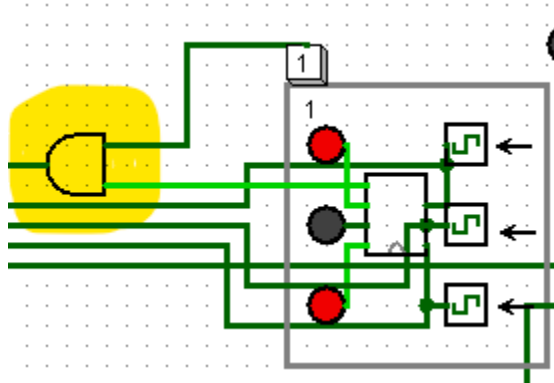The input for the next component will be the AND of the button input (which is 1) as long as it is pressed and the availability of free slot in that block  
 If a free slot is available, it returns 1, so when the button is pressed, input will be 1&1 which is 1




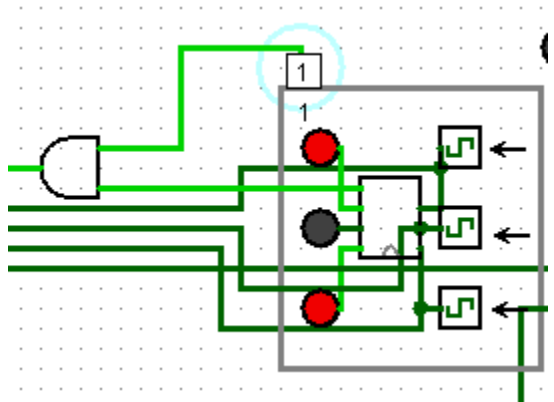As we can see, only 3 slots are filled as per the leds  
 Which means a free slot is available  
 And when the button is pressed, the output is 1



What will happen after this button press is that the path to this block will be displayed by the junctions which is triggered by the 1 output which we get when the button is pressed.

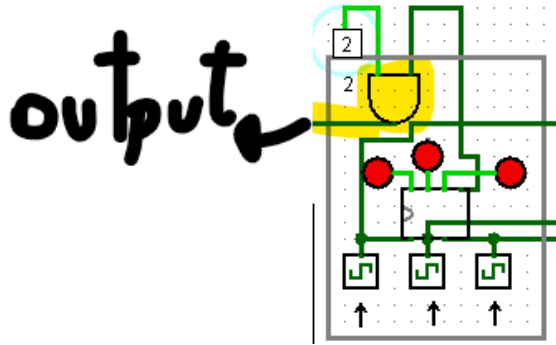If no free slot is available, it returns 0, so when the button is pressed, input will be 1&0 which is 0, i.e. there is no change in the circuit and input from this side will remain 0.  
 By default, the input from this block will be 0.



As we can see, bcos all 3 leds are blinking, no free slot is available, so even though the button is pressed, the output will be 0.


Bcos, there is not change in the output, pressing the button in this situation wont change anything


Bcos this block is filled, a path to this block wont be shown

This input is connected to the BlockChooser

The input from Block i is connected to the ith port of BlockChooser

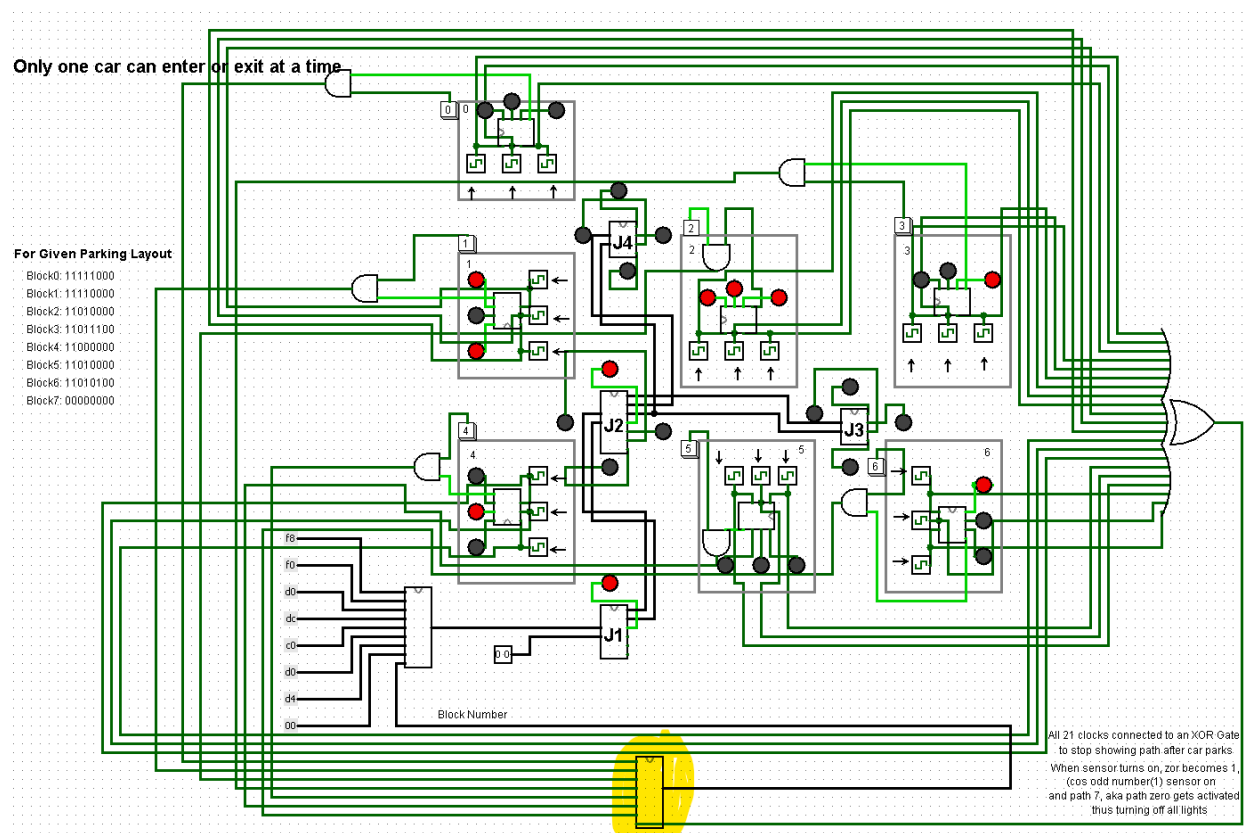The Block Chooser will eventually return the BlockNumber of the most recent button which is pressed.



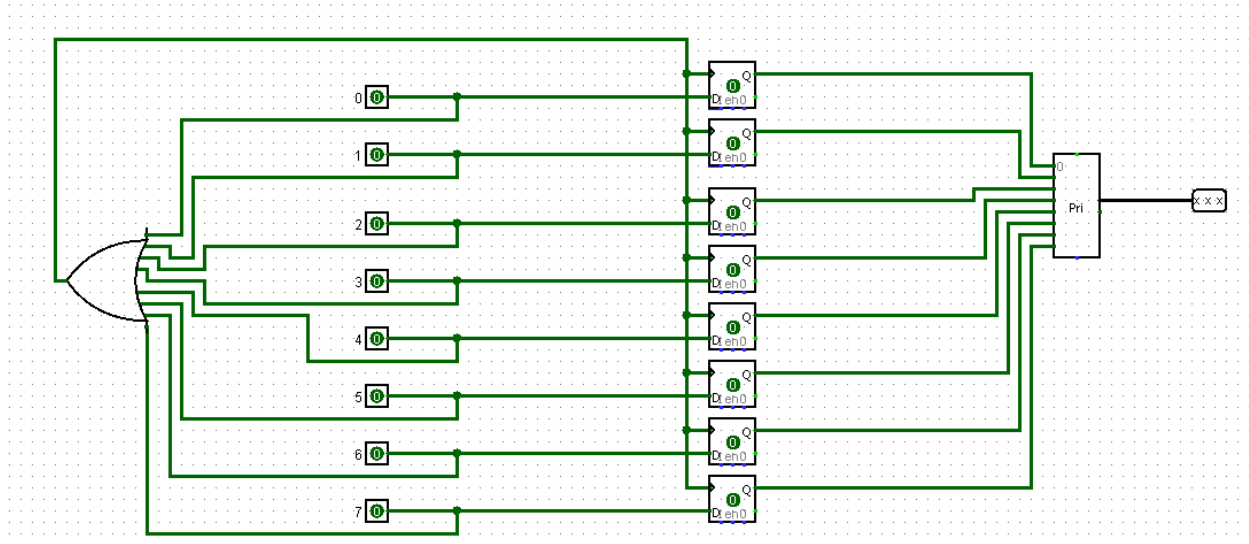

How this works is


If button 2 was pressed, the input 2 becomes 1

And simultaneously the clock tick for each flipflop changes from 0 to 1


Bcos the OR gate whose output was initially 0

Returns 1 now

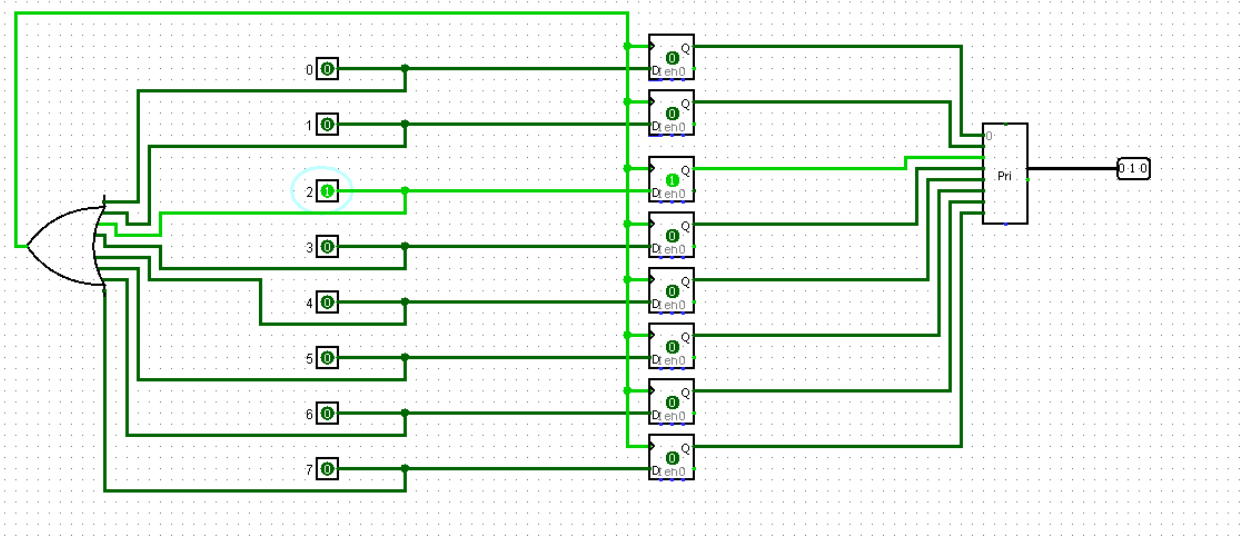And the output for the flipflop connected to input 2, becomes 1



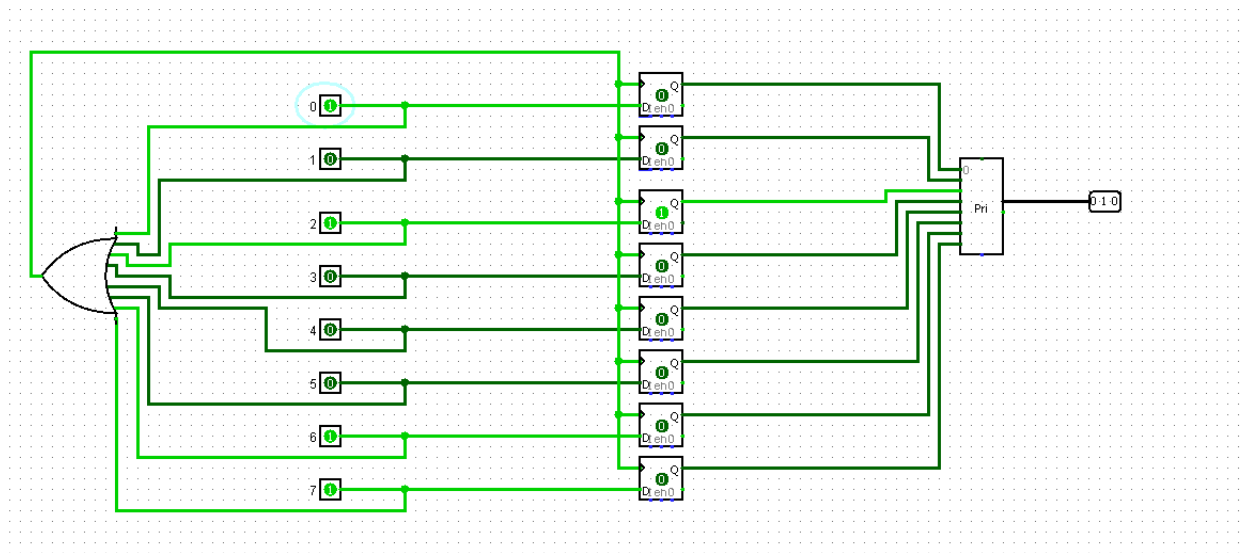Now, bcos the clock is not ticking and fixed at 1, even if the user presses multiple buttons, only the 2nd flipflop output will be considered, bcos until the next clock tick, the previous output will be displayed, bcos the OR gate still remains at 1 for the added 1 inputs, the clock tick doesnt change and is still at 1



Now, after the path is generated, which will be explained later

The user will leave,


So he is not pressing any button now

after releasing the buttons

The OR gate returns 0 bcos all inputs are 0

So the next clock tick is activated

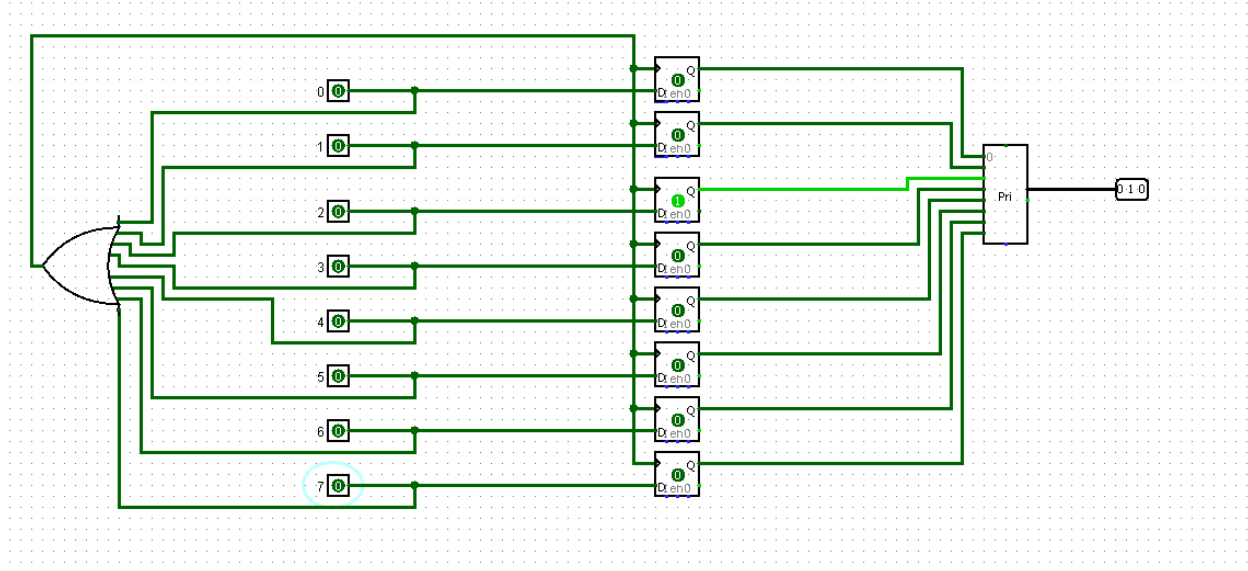So the previous input which is block 2 will be shown until another button is pressed



8 outputs connected from 8 D flipflops corresponding to their 8 respective inputs as per the above diagram will be taken as the corresponding inputs for the Priority Encoder

The Component marked Pri, is a Priority Encoder

Block 0 is input 0 in Pri

Block 1 is input 1 in Pri, and so on.....


Note: Block 7 is a special button whose functionality will be explained later on

The Priority Encoder gives Block Number in binary form as output

As we can see, after pressing the button for Block2, The block number is 010 which is the binary representation for Block2

The Block2 will be the output until another clock tick/change, i.e. another button is pressed, so the code will keep displaying the path for block2 until another button is pressed (which will be button 7, reason will be explained later)

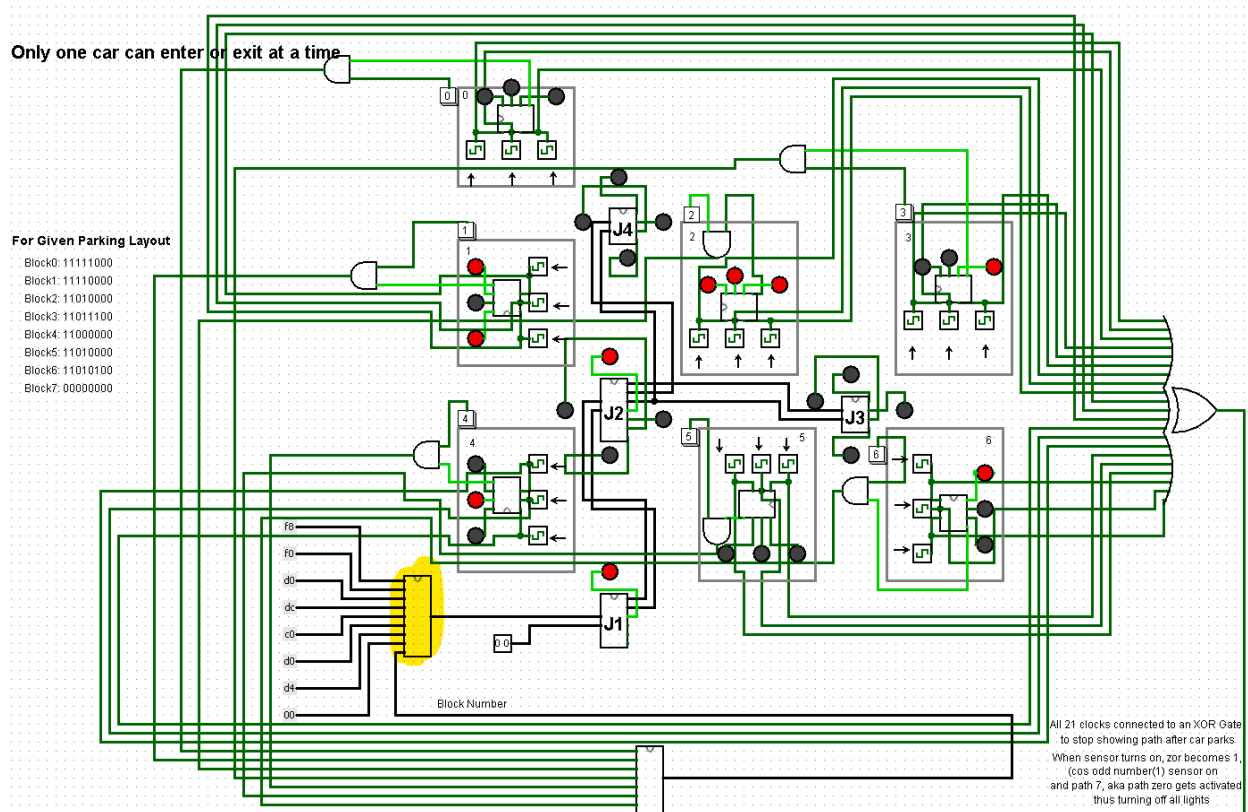
Now, this output block number will be taken as input for Path Generator



The highlighted component is PathGenerator

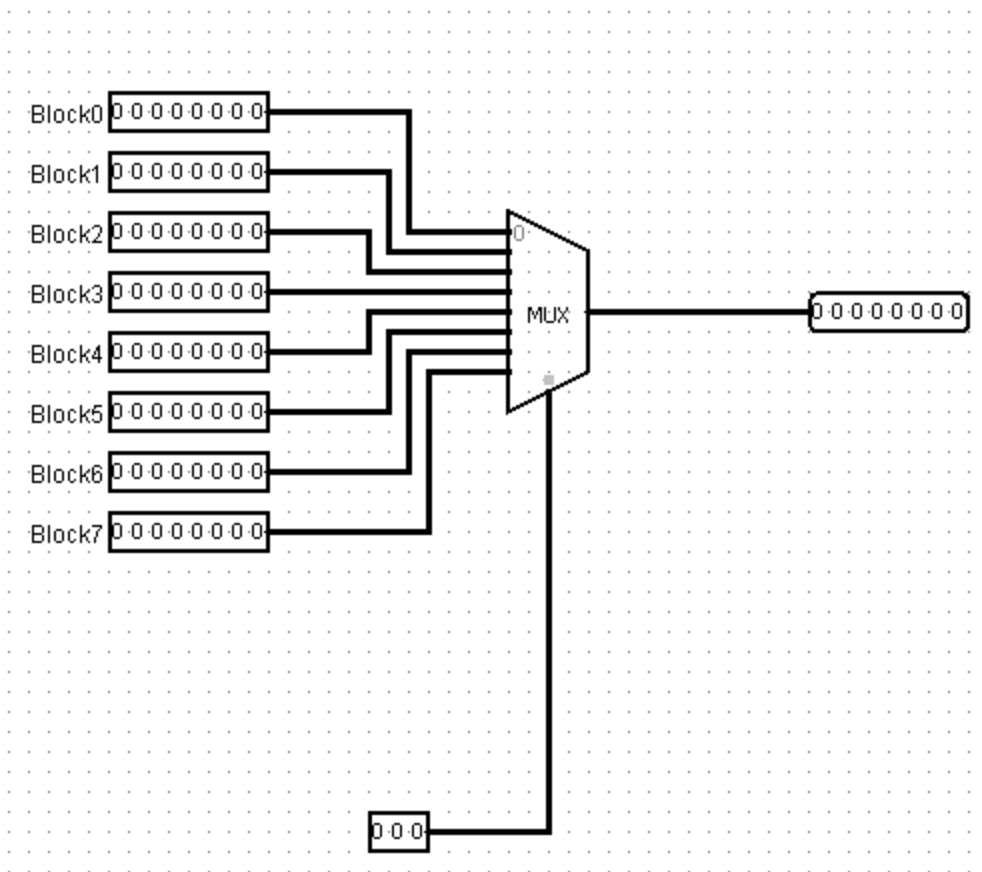The PathGenerator will give PathData as output which will be used by the junctions to display the path, i.e. which direction to go towards at each potential junction the user will encounter to go to that path.





This operation is preformed using a multiplexer

The Input at port k will be the PathData for Block Number k

And the select input will be block number

So, depending on the block number, the path is given

If the block number is 3, the PathData to reach Block 3 is an output

Same for all blocks.

This operation is preformed using a multiplexer

Now, let me explain what PathData means and what each junction is supposed to do and does for particular PathData. After doing so, i'll explain the junction layout for the above example.

The Path Generator will generate PathData to reach the particular Block Number  
PathData is essentially a 8 bit data, which gives information that represents a path.

The first 2 bits represent the direction to take at the first encountered junction  
The next 2 bits represent the direction to take at the second encountered junction  
The next 2 bits represent the direction to take at the third encountered junction  
And so on....

Note: At each junction,

We can extract the first 2 bits from PathData and call it direction

From the first 2 bits of PathData

11 represents front direction

10 represents left direction

01 represents right direction

00 is used for termination

(bcos we dont want the user to take a u-turn to reach their block, we dont use 00 to represent back direction. And after we reached all necessary junctions, the remaining PathData will be 00\_\_\_\_\_, reason will be explained later, so we dont want anymore junctions to display anything)

And left shift by 2, so that at next junction, we can use next 2 bits for direction

Let input direction signify the direction from which, each junction receives the input

With regards to input direction at the junction, let

00 represent south


01 represent west

10 represent east

11 represent north

Here is a truth table signifying which light (NORTH, SOUTH, EAST or WEST) of the junction must be displayed depending on input direction and

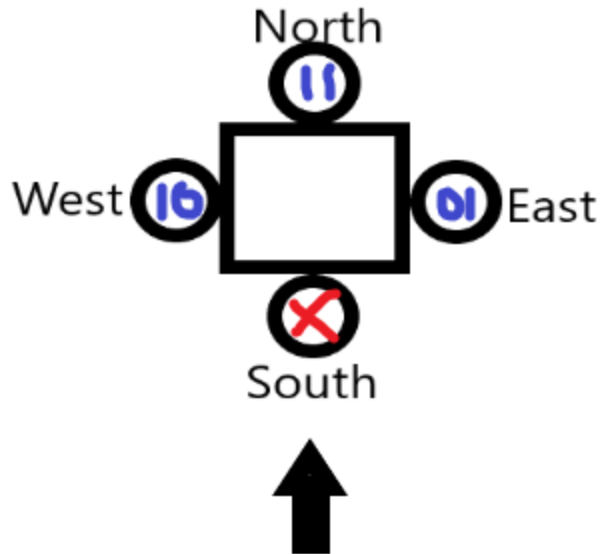Depending on direction of encountering the junction and the direction displayed based on the 2 data input, here is a truth table




In this direction, input direction is 00, i.e. south

If input is 11, we must go front from south direction which signifies north, north light is on

If Input is 10, we must go left from south direction which signifies west, west light is on

If Input is 01, we must go right from south direction which signified east, east light is on

If input is 00, no light will be on

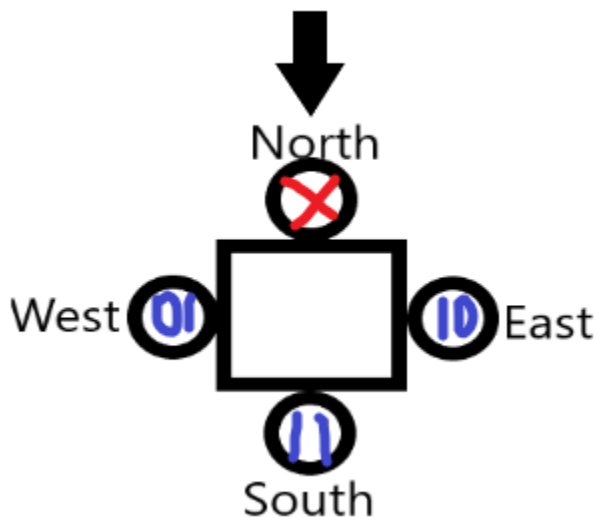


In this direction, input direction is 11, i.e. north

If input is 11, we must go front from north direction which signifies south, south light is on

If Input is 10, we must go left from north direction which signifies east, east light is on

If Input is 01, we must go right from north direction which signified west, west light is on

If input is 00, no light will be on

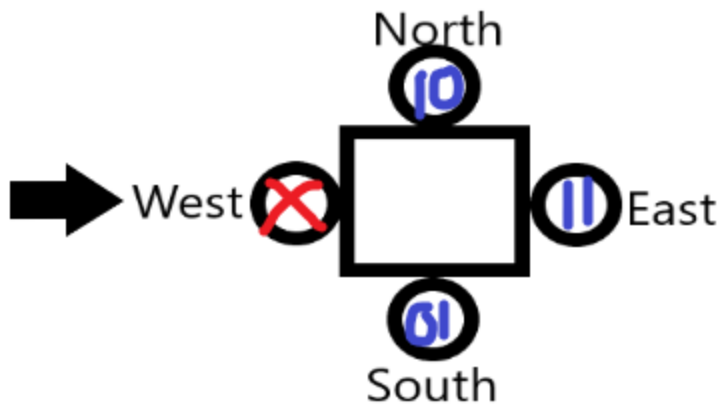


In this direction, input direction is 10, i.e. west

If input is 11, we must go front from west direction which signifies east, east light is on

If Input is 10, we must go left from west direction which signifies north, north light is on

If input is 00, no light will be on

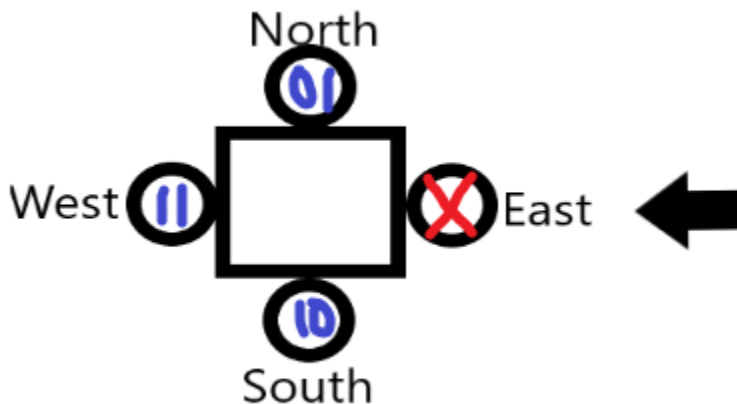

In this direction, input direction is 10, i.e. east

If input is 11, we must go front from east direction which signifies west, west light is on

If Input is 10, we must go left from east direction which signifies south, south light is on

If Input is 01, we must go right from east direction which signifies north, north light is on

If input is 00, no light will be on

Let us assume display is 0 when direction from pathdata is 00 to make simplification easier,

We can and each light with display so that nothing is displayed when display is 0

So  $dis = dir[0] \& dir[1];$

Here is a truth table signifying the same

Input Direction	Direction from PathData	North Light	South Light	East Light	West Light
_00	_00	0	1	0	0
_00	_01	0	0	1	0
_00	10	0	0	0	1
_00	11	1	0	0	0
11	_00	1	0	0	0
11	_01	0	0	0	1
11	10	0	0	1	0
11	11	0	1	0	0
_01	_00	0	0	1	0
_01	_01	1	0	0	0
_01	10	0	1	0	0
_01	11	0	0	0	1
10	_00	0	0	0	1
10	_01	0	1	0	0
10	10	1	0	0	0
10	11	0	0	1	0

Using the same conventions for north as 11, south as 00, east as 01 and west as 10

I want the Output Direction be the input direction for the next junction

So, that if there is a junction with multiple outputs, we know what is the input direction for the next junction directly, so we don't need to initialize Input Direction for further junction except at Junction1 for entrance

So the light which must be displayed must be reverse to Output Direction

Therefore

North Light for Output Direction 00

South Light for Output Direction 11

East Light for Output direction 10

West Light for Output Direction 01

And i can decide whether the particular light must be outputted using this

```
assign NL = dis && (!OutputDir[1] && !OutputDir[0]);
```

```
assign SL = dis && (OutputDir[1] && OutputDir[0]);
```

```
assign EL = dis && (OutputDir[1] && !OutputDir[0]);
```

```
assign WL = dis && (!OutputDir[1] && OutputDir[0]);
```

If we don't encounter 00, dis will be 1

So the above and condition won't be affected

If we encounter a 00, no light is displayed

Cos all lights will give output 0 with dis as 0 in and gate

And, later on we'll see that if no light is displayed, the path is complete, thus we need not display anything,

Thus the next junction need not display anythin

so we can set the first two inputs of path data as 00 for the next junction

So that the next junction doesnt display anything

So truth table for Output Direction is opposite to the the Light which should be shown

Truth Table for Output Direction

Input Direction	Direction from PathData	Output Direction	
		OutputDir[1]	OutputDir[0]
_00	_00	1	1
_00	_01	1	0
_00	10	0	1
_00	11	0	0
11	_00	0	0
11	_01	0	1
11	10	1	0
11	11	1	1
_01	_00	1	0
_01	_01	0	0
_01	10	1	1
_01	11	0	1
10	_00	0	1
10	_01	1	1
10	10	0	0
10	11	1	0

K-Map for OutputDir[1] is

Input Direction

Direction

	_00	_01	11	10
_00	1	1	0	0
_01	1	0	0	1
11	0	0	1	1
10	0	1	1	0

Note: if dir is 10, dir[1] is 1 & dir[0] is 0

The function is

```
assign OutputDir[1] = (!dir[1] && !dir[0] && !InputDir[1])
|| (!dir[1] && dir[0] && !InputDir[0])
|| (dir[1] && dir[0] && InputDir[1])
|| (dir[1] && !dir[0] && InputDir[0]);
```

Based on how the function is,

We can use a multiplexer

So the effective code is

```
mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);
```

Similarly, for OutputDirection[0]

As per truth table, the K-map is

Input Direction

Direction

	_00	_01	11	10
_00	1	0	0	1
_01	0	0	1	1
11	0	1	1	0
10	1	1	0	0

function is

```
assign OutputDir[0] = (!dir[1] && !dir[0] && !InputDir[0])
```

```

|| (!dir[1] && dir[0] && InputDir[1])
|| (dir[1] && dir[0] && InputDir[0])
|| (dir[1] && !dir[0] && !InputDir[1]);

```

Based on how the function is,

We can use a multiplexer

So the effective code is

```

mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);

```

After this, if the next junction is at the left

For the junction at left

The code returns the shifted path data, after left shift of 2

```

assign NewPath = PathData << 2;

```

Note that, each junction can receive input from only one direction.

We are doing so to optimize the project by the usage of a lesser number of components.

To do so, we need to ensure that the chosen PathDatas adhere with the above conditions.

So, what we do is, when we choose the path data, we ensure that, in every PathData, if a junction is to be encountered, the path to that junction will be unique.

Which means, the input direction to that junction will be unique,

Therefore, only one input direction for each junction.

This is the path data for each block for the parking layout

```

Block0: 11111000
Block1: 11110000
Block2: 11010000
Block3: 11011100
Block4: 11000000
Block5: 11010000
Block6: 11010100
Block7: 00000000


```

And this is the parking layout:



Junc	Path from Junc
2	11
3	1101
4	1111

Block	Path
0	11110000
1	11110000
2	11010000
3	11011100
4	11000000
5	11010000
6	11010100

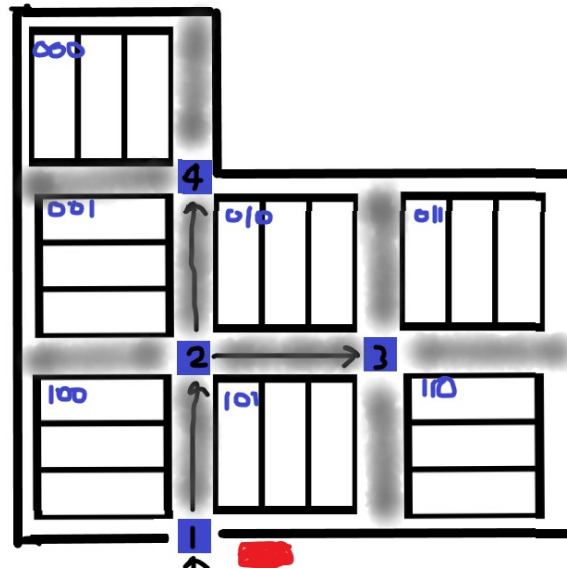

Now for our layout

Junction 1 passes New Pathdata to Junction 2 from south direction

If north light is displayed, it means we are supposed to go to junction 2

So the first 2 characters will remain the same in NewPath, so for junction1

(We make first 2 characters 00 if we are not supposed to go in that direction, in this case, when North Light is 00)

```
Junction1 j1(InputDir,PathData,NL1,SL1,EL1,WL1,OutputDir1,NewPath1);
  assign InputDir2 = OutputDir1;
  assign PathData2[7] = NewPath1[7] && NL1;
  assign PathData2[6] = NewPath1[6] && NL1;
  assign PathData2[5:0] = NewPath1[5:0];
```

Junction 2 passes New Pathdata to Junction 3 from west direction is east light is on

And Junction4 from north direction if north light is on

If East light is on, the next junction we must go to is Junction 3

So we can and the first two digits of NewPath of Junction3 with the East Light so that for junction3, pathdata will give output based on next two digits in Path data

Because we are doing and with east lights,

If the north light was switched on and east light was switched off, we were not supposed to go to junction3

So the NewPath for Junction3's first 2 digits will be 00

Which means, nothing will be displayed at Junction3

We similarly do the same with North Light for Junction4

```

Junction2 j2(InputDir2,PathData2,NL2,SL2,EL2,WL2,OutputDir2,NewPath2);
assign InputDir3 = OutputDir2;
assign PathData3[7] = NewPath2[7] && EL2;
assign PathData3[6] = NewPath2[6] && EL2;
assign PathData3[5:0] = NewPath2[5:0];
assign InputDir4 = OutputDir2;
assign PathData4[7] = NewPath2[7] && NL2;
assign PathData4[6] = NewPath2[6] && NL2;
assign PathData4[5:0] = NewPath2[5:0];

```


Junction 3 and 4 doesn't pass New Pathdata to any junction  
So the code for them is

```

Junction3 j3(InputDir3,PathData3,NL3,SL3,EL3,WL3);
Junction4 j4(InputDir4,PathData4,NL4,SL4,EL4,WL4);

```

Let us assume the PathData is 11111000

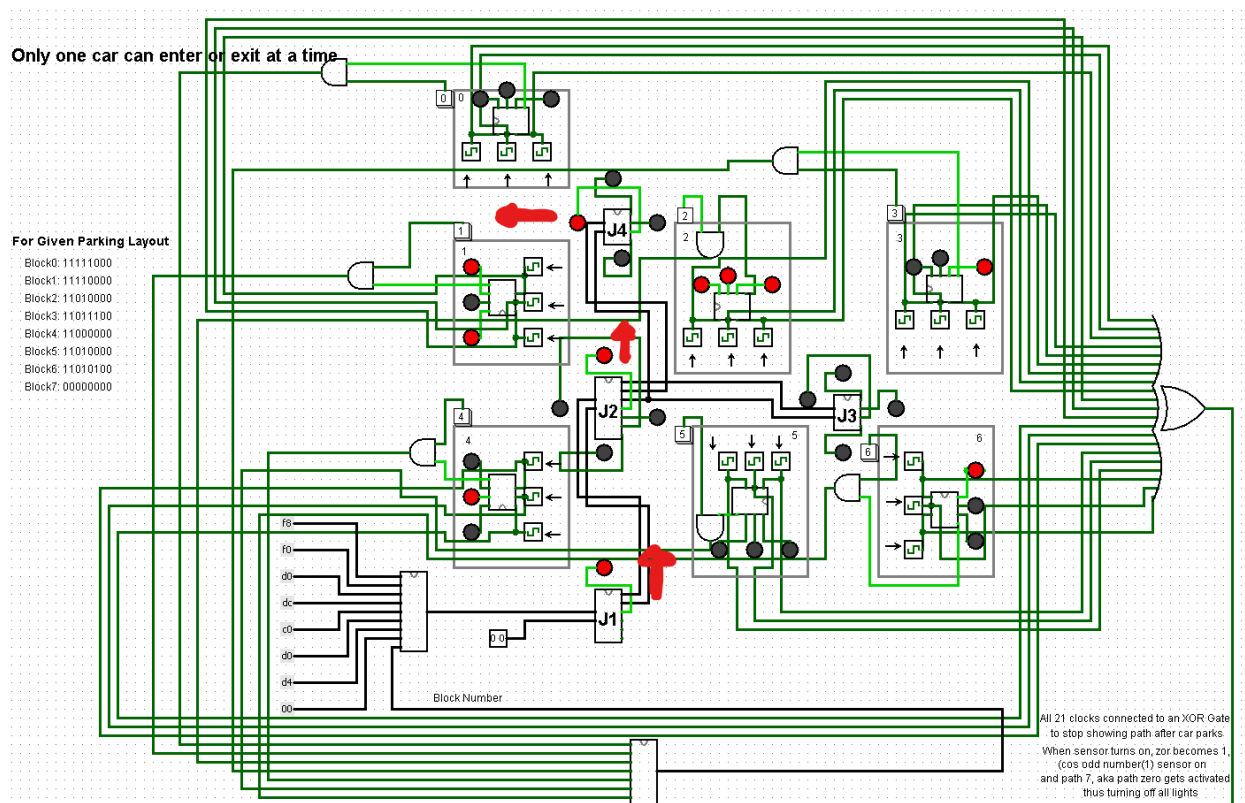

In this case, the PathData to Block0 is 11111000

As we can see

We will encounter junction1 from the south, so input direction is 00 and at junction1, we consider the first 2 bits from PathData which is 11

Junction displays north light

After left shift, new pathdata is 11100000 for junction 2

We will encounter junction2 from the south, so input direction is 00 and at junction2, we consider the first 2 bits from PathData which is 11

Junction displays north light

Because we chose north light

We pass data to junction 4 and 0s to junction 3

Due to which junction 3 doesn't display anything

After left shift, new pathdata is 10000000 for junction 4

As we can see

We will encounter junction1 from the south, so input direction is 00 and at junction1, we consider the first 2 bits from PathData which is 10

Junction displays east light

There are no more junction, so code ends


Now, for the Car sensors,

Let us take an example

Now, when the user enters the 3rd slot at block2

The third sensor(clock), which is present at the entrance of the slot turns on

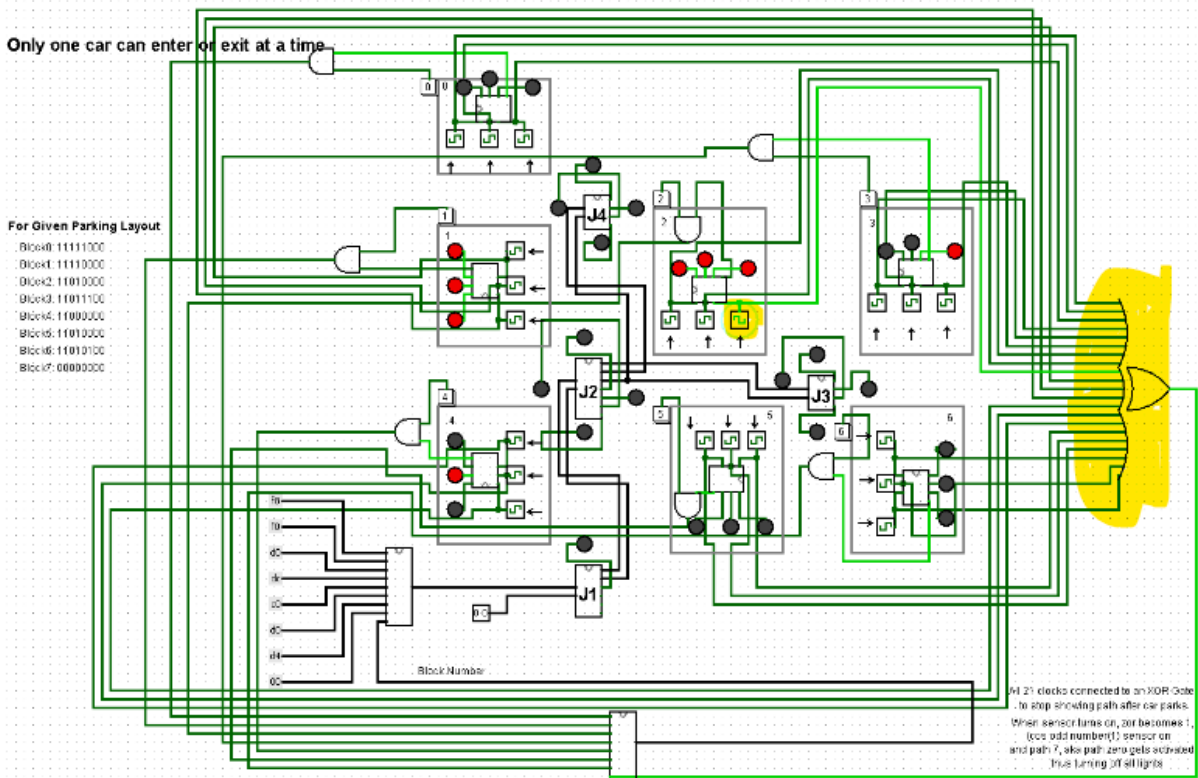Which means, the person is going to enter in that slot



Now that this clock is turned on, the path towards block2 disappears  
Bcos the car will be parked in this slot now, and thus doesnt need the directions anymore

This is done by using button7 which will always display path 00000000 through which none of the junctions display anything  
This button input is connected for port7 in block chooser

Button 7 is an xor gate to all 21 clocks  
Earlier all clocks were 0, so 0 1s, even parity, so XOR returns 0  
So button 7 is not chosen

NOTE: just saying button, but it is not really a button

But when that clock is turned on while car is entering  
1 clock shows 1, so 1 1 times, odd parity, so XOR returns 1  
So button 7 is chosen, and as mentioned earlier, all junctions don't display anything


Once the car parks in that slot  
He will cross the entrance of that slot  
Thus, the sensor(clock) for that slot becomes 0 again

Button 7 is an xor gate to all 21 clocks

again all clocks were 0, so 0 1s, even parity, so XOR returns 0

So button 7 is not chosen

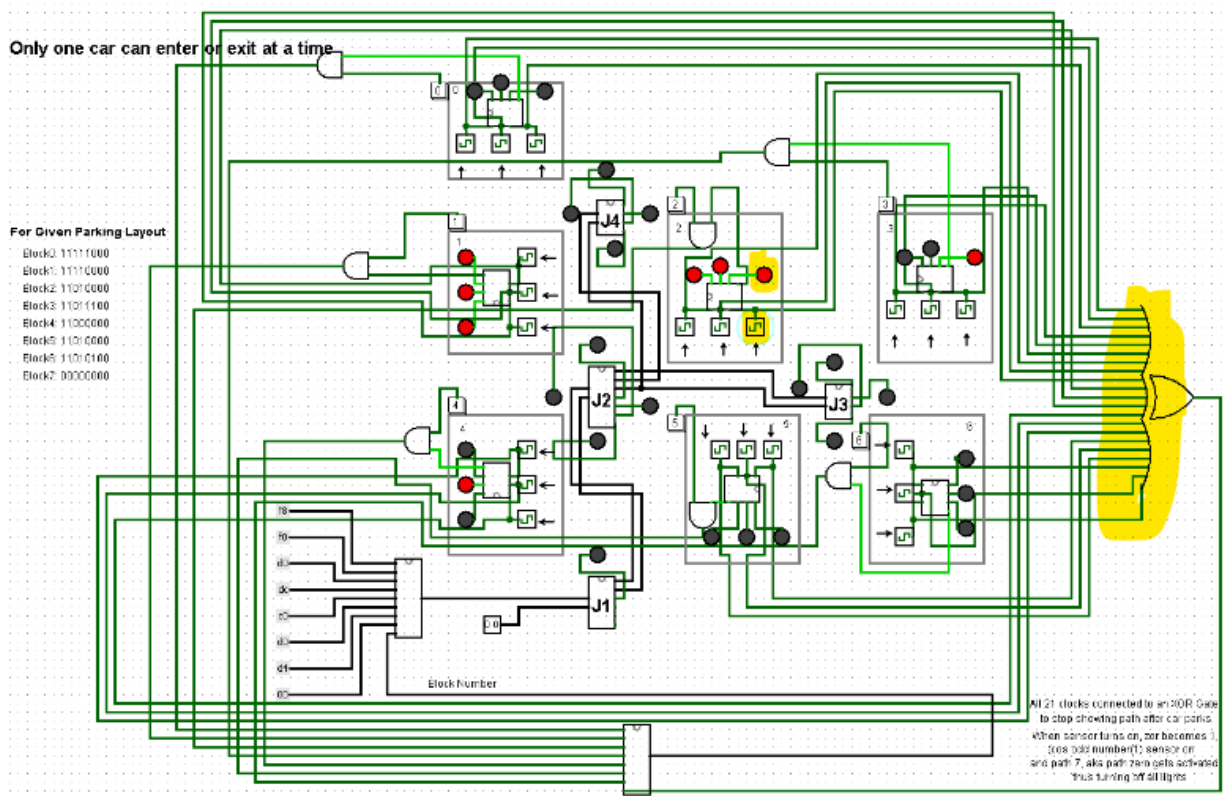So as per the PathChooser code, the output is block7 for which all junctions still display nothing




As we can see,


Now, on the screen we can see that the third slot of block 2 which was previously empty is now full as displayed by the LED after the current user parked in that slot

## Logisim Circuit Diagram:


### Basic Junction Circuit

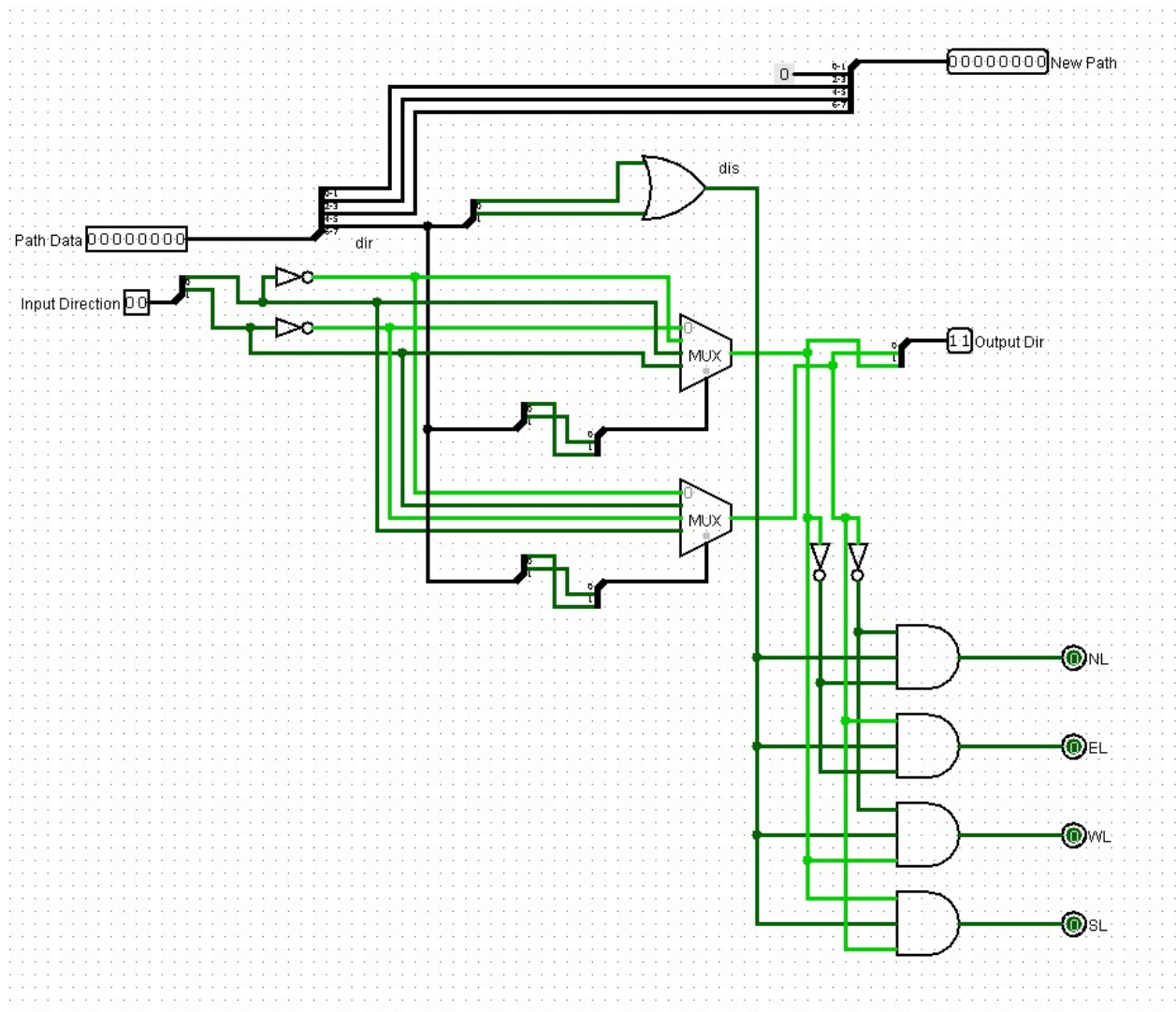

### Junction1

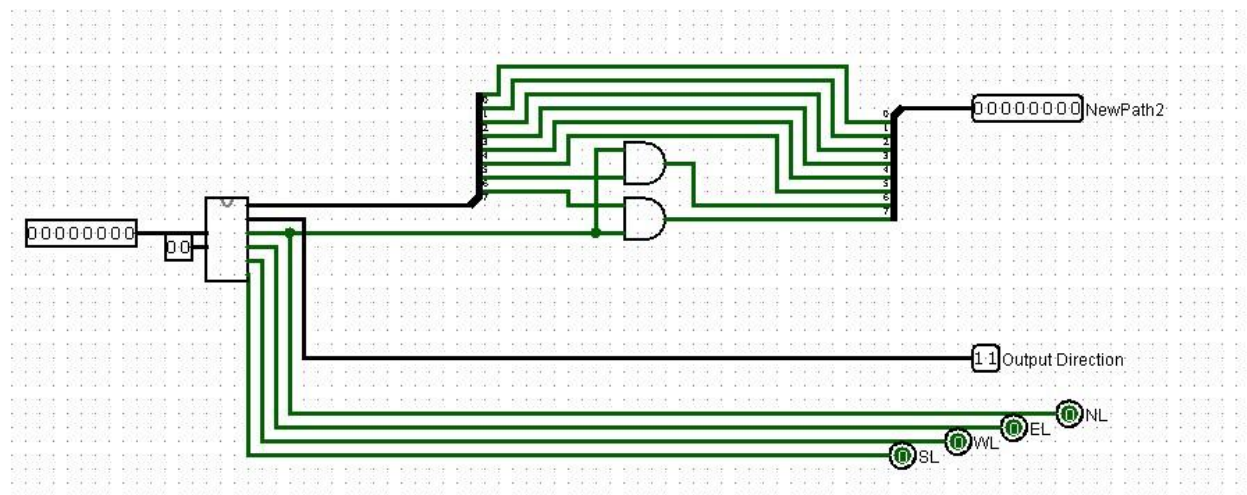

Junction2

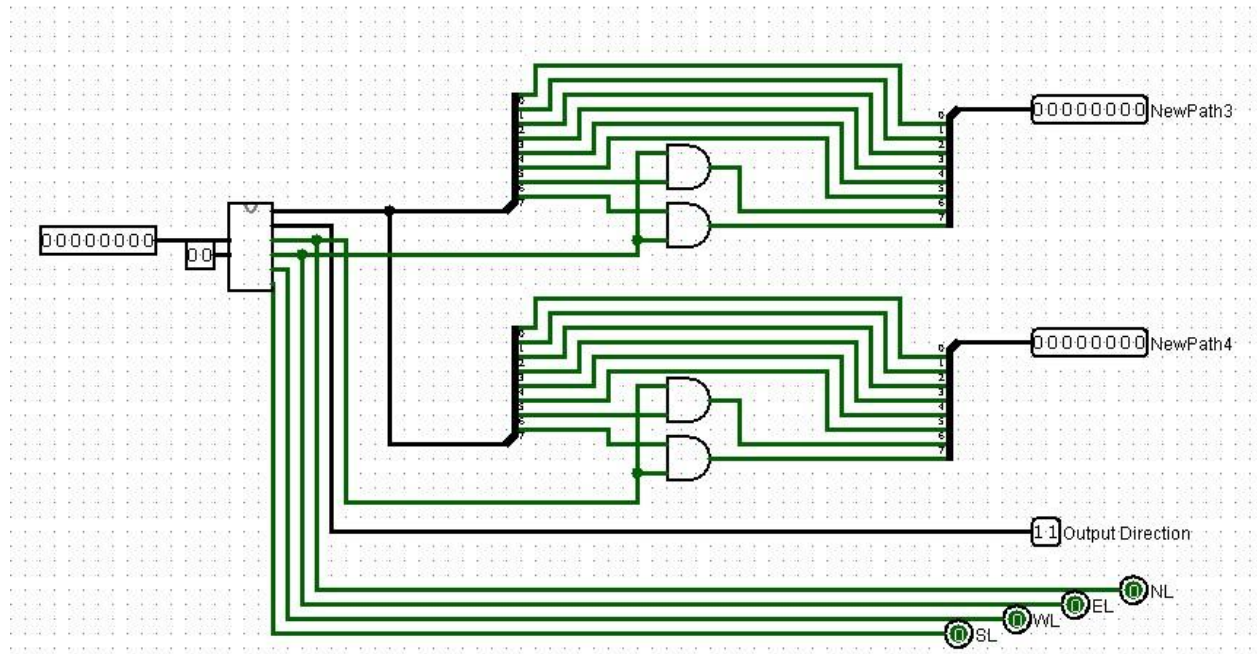


Junction3






## Junction4

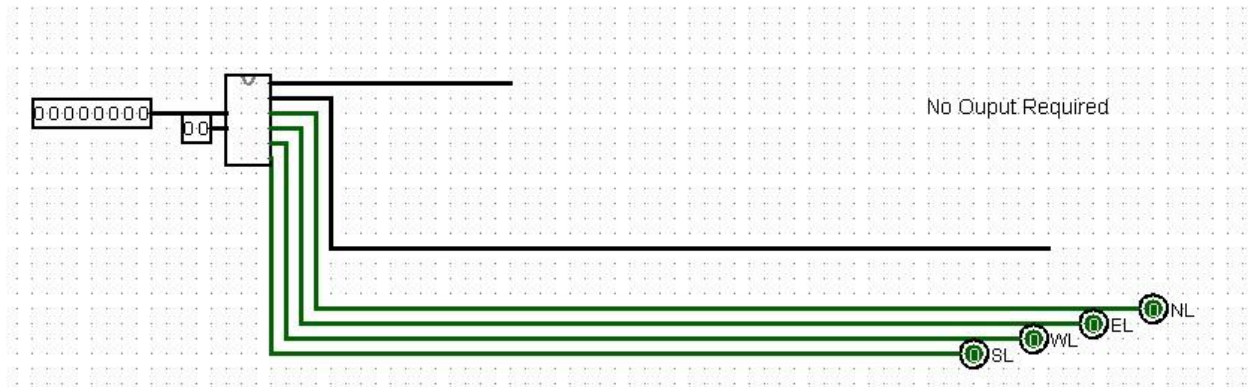


## Car Sensor

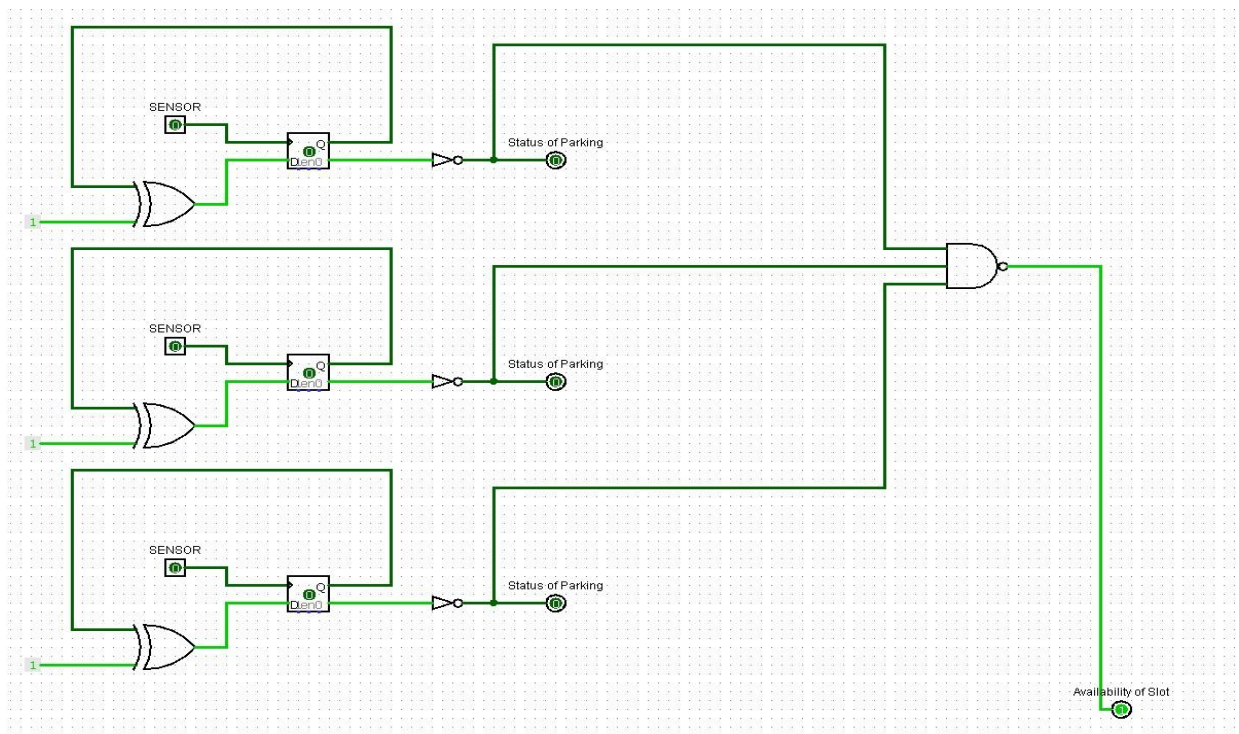


## PathGenerator




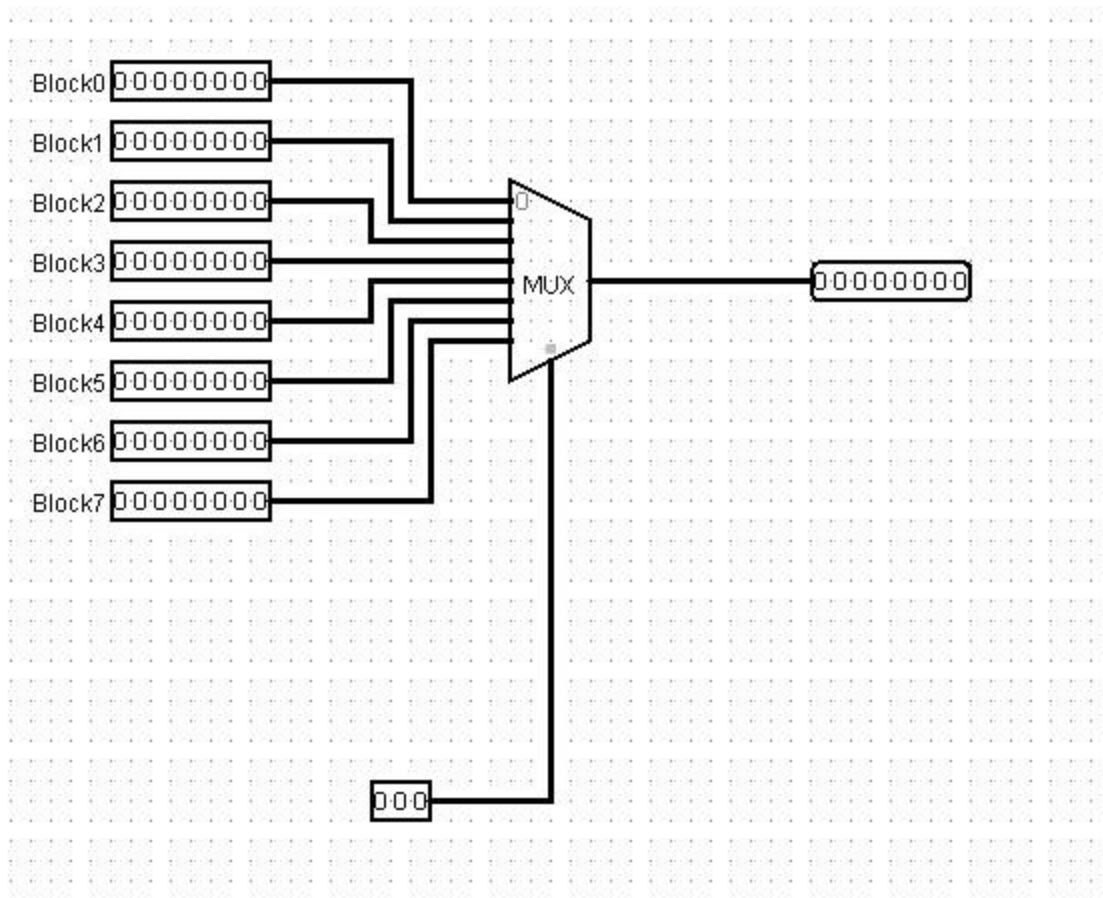

## BlockChooser

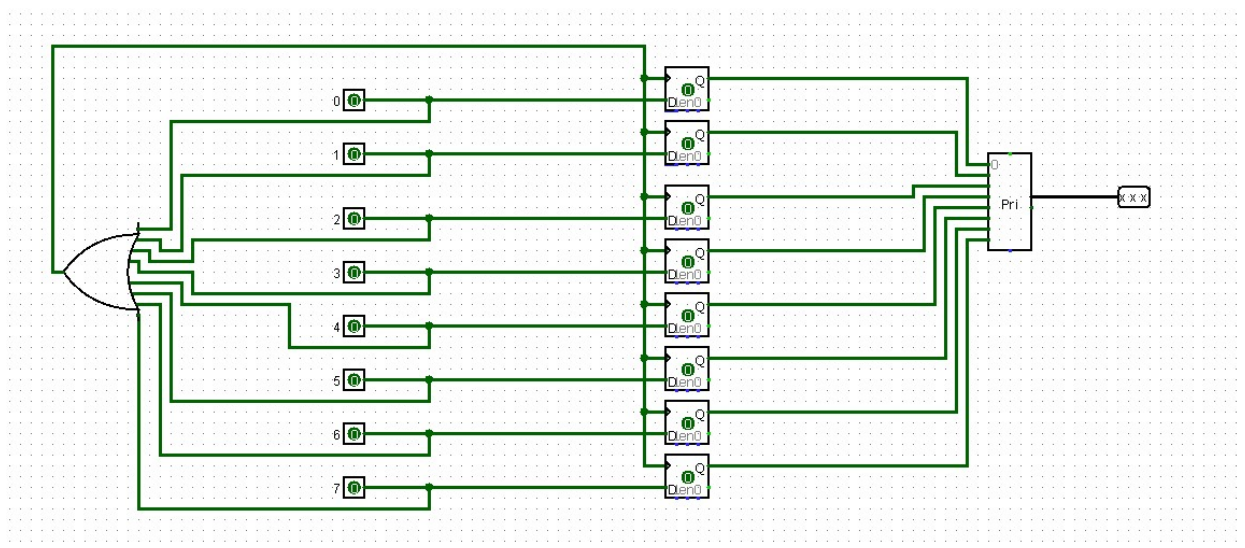

## Final Circuit Diagram

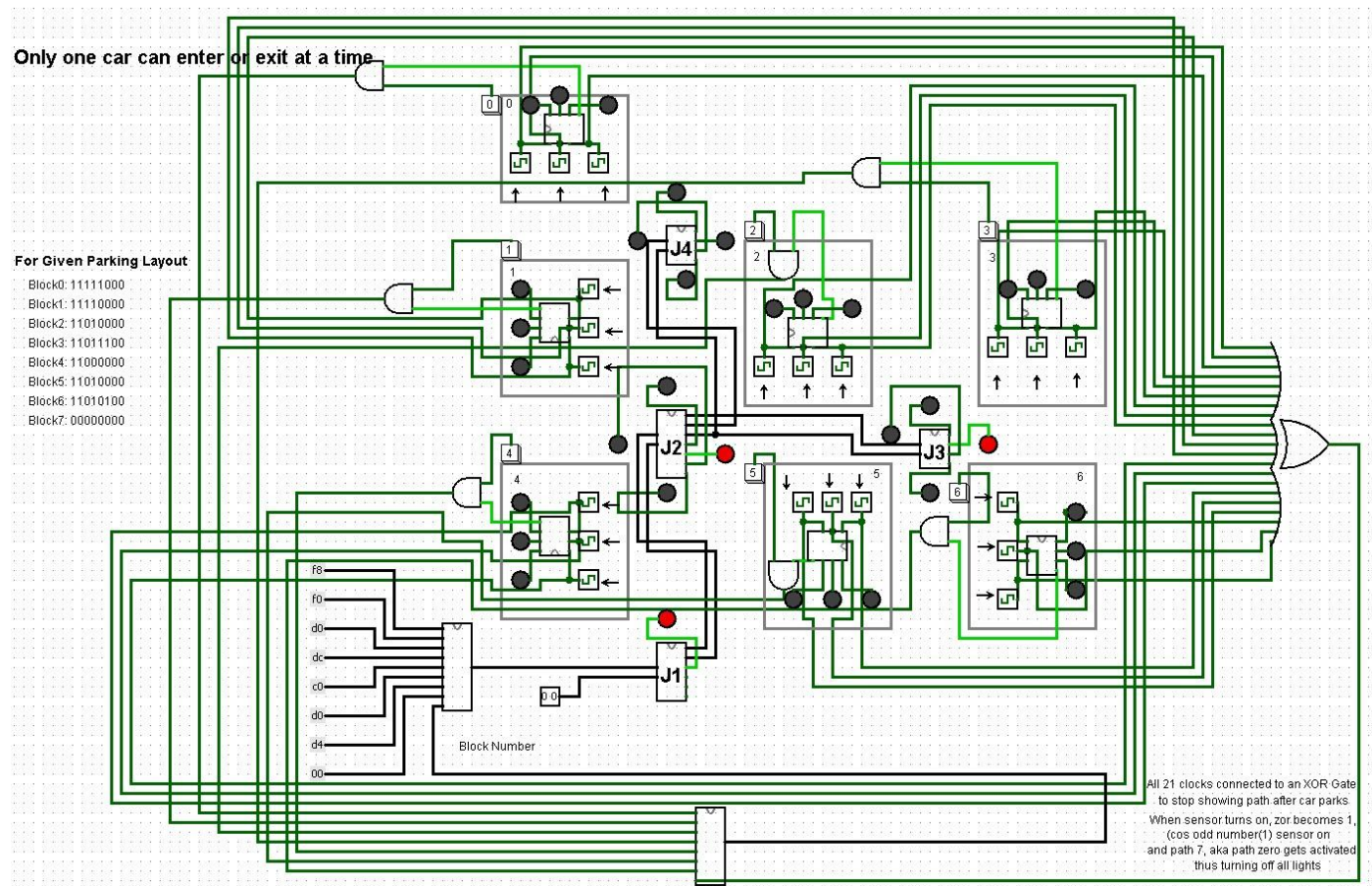

## Verilog Codes:

### Junction Code

```
module mux(a,b,c,d,sel,out); // 4*1 mux
```

```
input a,b,c,d;
input [1:0]sel;
output out;
```

```
assign out = (!sel[1] && !sel[0] && a)
             || (!sel[1] && sel[0] && b)
             || (sel[1] && !sel[0] && c)
             || (sel[1] && sel[0] && d);
```

```
endmodule
```

```
module Junction4(InputDir,PathData,NL,SL,EL,WL);  
    input [1:0]InputDir;  
    output [1:0]OutputDir;  
    input [7:0]PathData;  
    output [7:0]NewPath;  
    output NL,SL,EL,WL;  
  
    wire [1:0]dir;  
    assign dir = PathData[7:6];  
  
    wire dis;  
    assign dis = dir[0] || dir[1];  
  
    mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);  
    mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);  
  
    assign NL = dis && (!OutputDir[1] && !OutputDir[0]);  
    assign SL = dis && (OutputDir[1] && OutputDir[0]);  
    assign EL = dis && (OutputDir[1] && !OutputDir[0]);  
    assign WL = dis && (!OutputDir[1] && OutputDir[0]);  
  
    assign NewPath = PathData << 2;
```

```
endmodule
```

```
module Junction4_tb;  
  
    reg [1:0] InputDir;  
    reg [7:0] PathData;  
    wire NL, SL, EL, WL;  
    wire [1:0] OutputDir;  
  
    Junction4 uut (InputDir,PathData,NL,SL,EL,WL);  
  
    initial begin
```

```

$dumpfile("Junction4.vcd");
$dumpvars(0, Junction4_tb);

$display("-----");
$display("| InputDir | PathData | NL | SL | EL | WL |");
$display("-----");
$monitor("| %b | %b | %b | %b | %b | %b |",
         InputDir, PathData, NL, SL, EL, WL);

```

```

InputDir = 2'b00;
PathData = 8'b00000000;
#10 PathData = 8'b01000000;
#20 PathData = 8'b10000000;
#30 PathData = 8'b11000000;

```

```

#40
InputDir = 2'b11;
PathData = 8'b00000000;
#50 PathData = 8'b01000000;
#60 PathData = 8'b10000000;
#70 PathData = 8'b11000000;

```

```

#80
InputDir = 2'b01;
PathData = 8'b00000000;
#90 PathData = 8'b01000000;
#100 PathData = 8'b10000000;
#110 PathData = 8'b11000000;

```

```

#120
InputDir = 2'b10;
PathData = 8'b00000000;
#130 PathData = 8'b01000000;
#140 PathData = 8'b10000000;
#150 PathData = 8'b11000000;

```

```

#1000 $display("-----");

```

```

end
endmodule

```

## Junction Simulation Code

//We choose path data such that there is only one unique input direction to each junction

// Eg. The only path to Junction3 is 1101, 11 at Junction1 and 01 at Junction2

// Junction3 can only receive input from Junction2

//Block input will be given from the Button code

module

Display(Block,PathData,NL1,SL1,EL1,WL1,NL2,SL2,EL2,WL2,NL3,SL3,EL3,WL3,NL4,SL4,EL4,WL4);

input [2:0]Block;  
wire [1:0]InputDir;  
output [7:0]PathData;

assign InputDir=2'b00;  
PathFinder m1(Block,PathData);

output NL1,SL1,EL1,WL1,NL2,SL2,EL2,WL2,NL3,SL3,EL3,WL3,NL4,SL4,EL4,WL4;

wire [1:0]InputDir2,InputDir3,InputDir4;  
wire [1:0]OutputDir1,OutputDir2;  
wire [7:0]NewPath1,NewPath2;  
wire [7:0]PathData2,PathData3,PathData4;

Junction1 j1(InputDir,PathData,NL1,SL1,EL1,WL1,OutputDir1,NewPath1);  
assign InputDir2 = OutputDir1;  
assign PathData2[7] = NewPath1[7] && NL1;  
assign PathData2[6] = NewPath1[6] && NL1;  
assign PathData2[5:0] = NewPath1[5:0];

Junction2 j2(InputDir2,PathData2,NL2,SL2,EL2,WL2,OutputDir2,NewPath2);  
assign InputDir3 = OutputDir2;  
assign PathData3[7] = NewPath2[7] && EL2;  
assign PathData3[6] = NewPath2[6] && EL2;  
assign PathData3[5:0] = NewPath2[5:0];  
assign InputDir4 = OutputDir2;  
assign PathData4[7] = NewPath2[7] && NL2;

```
assign PathData4[6] = NewPath2[6] && NL2;  
assign PathData4[5:0] = NewPath2[5:0];
```

```
Junction3 j3(InputDir3,PathData3,NL3,SL3,EL3,WL3);  
Junction4 j4(InputDir4,PathData4,NL4,SL4,EL4,WL4);
```

```
endmodule
```

```
//Multiplexer for each out index required for Pathfinder  
module mux1(a,i0,i1,i2,i3,i4,i5,i6,i7,o);
```

```
input [2:0]a;  
input i0,i1,i2,i3,i4,i5,i6,i7;  
output o;
```

```
assign o = (!a[2] && !a[1] && !a[0] && i0) ||  
           (!a[2] && !a[1] && a[0] && i1) ||  
           (!a[2] && a[1] && !a[0] && i2) ||  
           (!a[2] && a[1] && a[0] && i3) ||  
           (a[2] && !a[1] && !a[0] && i4) ||  
           (a[2] && !a[1] && a[0] && i5) ||  
           (a[2] && a[1] && !a[0] && i6) ||  
           (a[2] && a[1] && a[0] && i7);
```

```
endmodule
```

```
module Pathfinder(a,out);    //Like 8*1 mux
```

```
input [2:0]a;  
output [7:0]out;  
wire [7:0]a0,a1,a2,a3,a4,a5,a6,a7;
```

```
assign a0=8'b11111000;  
assign a1=8'b11110000;  
assign a2=8'b11010000;  
assign a3=8'b11011100;  
assign a4=8'b11000000;  
assign a5=8'b11010000;  
assign a6=8'b11010100;  
assign a7=8'b00000000;
```

```

mux1 m7(a,a0[7],a1[7],a2[7],a3[7],a4[7],a5[7],a6[7],a7[7],out[7]);
mux1 m6(a,a0[6],a1[6],a2[6],a3[6],a4[6],a5[6],a6[6],a7[6],out[6]);
mux1 m5(a,a0[5],a1[5],a2[5],a3[5],a4[5],a5[5],a6[5],a7[5],out[5]);
mux1 m4(a,a0[4],a1[4],a2[4],a3[4],a4[4],a5[4],a6[4],a7[4],out[4]);
mux1 m3(a,a0[3],a1[3],a2[3],a3[3],a4[3],a5[3],a6[3],a7[3],out[3]);
mux1 m2(a,a0[2],a1[2],a2[2],a3[2],a4[2],a5[2],a6[2],a7[2],out[2]);

```

```

assign out[1]=1'b0;
assign out[0]=1'b0;

```

```

endmodule

```

```

module mux(a,b,c,d,sel,out); // 4*1 mux

```

```

input a,b,c,d;
input [1:0]sel;
output out;

```

```

assign out = (!sel[1] && !sel[0] && a)
             || (!sel[1] && sel[0] && b)
             || (sel[1] && !sel[0] && c)
             || (sel[1] && sel[0] && d);

```

```

endmodule

```

```

module Junction1(InputDir,PathData,NL,SL,EL,WL,OutputDir,NewPath);
    input [1:0]InputDir;
    output [1:0]OutputDir;
    input [7:0]PathData;
    output [7:0]NewPath;
    output NL,SL,EL,WL;

    wire [1:0]dir;
    assign dir = PathData[7:6];

    wire dis;
    assign dis = dir[0] || dir[1];

```

```
mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);
mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);
```

```
assign NL = dis && (!OutputDir[1] && !OutputDir[0]);
assign SL = dis && (OutputDir[1] && OutputDir[0]);
assign EL = dis && (OutputDir[1] && !OutputDir[0]);
assign WL = dis && (!OutputDir[1] && OutputDir[0]);
```

```
assign NewPath = PathData << 2;
```

```
endmodule
```

```
module Junction2(InputDir,PathData,NL,SL,EL,WL,OutputDir,NewPath);
    input [1:0]InputDir;
    output [1:0]OutputDir;
    input [7:0]PathData;
    output [7:0]NewPath;
    output NL,SL,EL,WL;
```

```
    wire [1:0]dir;
    assign dir = PathData[7:6];
```

```
    wire dis;
    assign dis = dir[0] || dir[1];
```

```
    mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);
    mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);
```

```
    assign NL = dis && (!OutputDir[1] && !OutputDir[0]);
    assign SL = dis && (OutputDir[1] && OutputDir[0]);
    assign EL = dis && (OutputDir[1] && !OutputDir[0]);
    assign WL = dis && (!OutputDir[1] && OutputDir[0]);
```

```
    assign NewPath = PathData << 2;
```

```
endmodule
```

```
module Junction3(InputDir,PathData,NL,SL,EL,WL);
    input [1:0]InputDir;
```



```
output [1:0]OutputDir;  
input [7:0]PathData;  
output [7:0]NewPath;  
output NL,SL,EL,WL;
```

```
wire [1:0]dir;  
assign dir = PathData[7:6];
```

```
wire dis;  
assign dis = dir[0] || dir[1];
```

```
mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);  
mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);
```

```
assign NL = dis && (!OutputDir[1] && !OutputDir[0]);  
assign SL = dis && (OutputDir[1] && OutputDir[0]);  
assign EL = dis && (OutputDir[1] && !OutputDir[0]);  
assign WL = dis && (!OutputDir[1] && OutputDir[0]);
```

```
assign NewPath = PathData << 2;
```

```
endmodule
```

```
module Junction4(InputDir,PathData,NL,SL,EL,WL);
```

```
input [1:0]InputDir;  
output [1:0]OutputDir;  
input [7:0]PathData;  
output [7:0]NewPath;  
output NL,SL,EL,WL;
```

```
wire [1:0]dir;  
assign dir = PathData[7:6];
```

```
wire dis;  
assign dis = dir[0] || dir[1];
```

```
mux m1(!InputDir[1],!InputDir[0],InputDir[0],InputDir[1],dir,OutputDir[1]);  
mux m2(!InputDir[0],InputDir[1],!InputDir[1],InputDir[0],dir,OutputDir[0]);
```

```

assign NL = dis && (!OutputDir[1] && !OutputDir[0]);
assign SL = dis && (OutputDir[1] && OutputDir[0]);
assign EL = dis && (OutputDir[1] && !OutputDir[0]);
assign WL = dis && (!OutputDir[1] && OutputDir[0]);

```

```

assign NewPath = PathData << 2;

```

```

endmodule

```

```

module Display_tb;

```

```

    reg [2:0] Block;
    wire [7:0] PathData;
    wire NL1, SL1, EL1, WL1;
    wire NL2, SL2, EL2, WL2;
    wire NL3, SL3, EL3, WL3;
    wire NL4, SL4, EL4, WL4;

```

```

    Display
    d1(Block,PathData,NL1,SL1,EL1,WL1,NL2,SL2,EL2,WL2,NL3,SL3,EL3,WL3,NL4,SL4,
    EL4,WL4);

```

```

    initial begin
        $dumpfile("Display.vcd");
        $dumpvars(0, Display_tb);

```

```

    $display("-----
    -----");

```

```

        $display("| Block | PathData | NL1 | SL1 | EL1 | WL1 | NL2 | SL2 | EL2 | WL2 | NL3
    | SL3 | EL3 | WL3 | NL4 | SL4 | EL4 | WL4 |");

```

```

    $display("-----
    -----");

```

```

        $monitor("| %b | %b | %b | %b | %b | %b | %b | %b | %b | %b | %b |
    %b | %b | %b | %b | %b | %b | %b |",

```

```

        Block, PathData, NL1, SL1, EL1, WL1, NL2, SL2, EL2, WL2, NL3, SL3, EL3,
        WL3, NL4, SL4, EL4, WL4);

```

```

Block=3'b000;
    repeat(7)
    begin
        #10 Block= Block + 3'b001;
    end

```

```

        #1000
$display("-----");
-----");

    end
endmodule

```

### Block Circuit Code

```

module dflipflop (input D, input CKT, output reg Q);
    always @(posedge CKT) begin
        Q <= D;
    end
endmodule

```

```

module block (input D1, input D2, input D3, input CKT1, input CKT2, input CKT3, output
Q1, output Q2, output Q3, output Free);
    wire Q1_wire, Q2_wire, Q3_wire;

    dflipflop s1 (.D(D1), .CKT(CKT1), .Q(Q1_wire));
    dflipflop s2 (.D(D2), .CKT(CKT2), .Q(Q2_wire));
    dflipflop s3 (.D(D3), .CKT(CKT3), .Q(Q3_wire));

    assign Q1 = Q1_wire;
    assign Q2 = Q2_wire;
    assign Q3 = Q3_wire;

    nand m1(Free, Q1,Q2,Q3);

```

```
endmodule
```

```
module block_tb;
```

```
reg D1,D2,D3,CKT1=0,CKT2=0,CKT3=0;
```

```
wire Q1,Q2,Q3,free;
```

```
block d(D1,D2,D3,CKT1,CKT2,CKT3,Q1,Q2,Q3,free);
```

```
always begin
```

```
    CKT1=~CKT1;
```

```
    #10;
```

```
end
```

```
always begin
```

```
    CKT2=~CKT2;
```

```
    #20;
```

```
end
```

```
always begin
```

```
    CKT3=~CKT3;
```

```
    #30;
```

```
end
```

```
initial begin
```

```
    $dumpfile("block.vcd");
```

```
    $dumpvars(0,block_tb);
```

```
end
```

```
initial begin
```

```
    $display("|Q1 |Q2 |Q3 |Free?|");
```

```
    $monitor("| %b | %b | %b | %b |",Q1,Q2,Q3,free);
```

```
    D1=1'b0;D2=1'b0;D3=1'b0;
```

```
    #20 D1=1'b1;
```

```
    #40 D2=1'b1;
```

```
    #60 D3=1'b1;
```

```
    #80 D1=1'b0;
```

```
    #100 D1=1'b1;
```

```
    #120 D1=1'b0;
```

```
    #140 D3=1'b0;
```

```
    #160 D2=1'b0;
```

```
end
```

```
initial #5000 $finish;
```

```
endmodule
```

### **Block Chooser Code**

```
//NOTE: Input B7 will be XOR of all sensors(clocks) present for each slot  
//The output block number will be the button number which is pressed last (when slot is  
empty, which is handled in logisim)  
//Bk is actually is button pressed & if free slot is available(from BlockCircuit code)  
//Note, simulation may not seem perfect since it is not that very feasible to simulate  
buttons through verilog
```

```
module dflipflop (input D, input CKT, output reg Q);  
    always @(posedge CKT) begin  
        Q <= D;  
    end  
endmodule
```

```
module PriorityEncoder(i,y);  
    input [7:0]i;  
    output [2:0]y;  
  
    assign y[2]=i[4] | i[5] | i[6] | i[7];  
    assign y[1]=i[2] | i[3] | i[6] | i[7];  
    assign y[0]=i[1] | i[3] | i[5] | i[7];  
  
endmodule
```

```
module BlockChooser(B,F);  
    input [7:0]B;  
    wire CKT;  
    wire [7:0]W;  
    output [2:0]F;  
  
    or O1(CKT,B[0],B[1],B[2],B[3],B[4],B[5],B[6],B[7]);  
  
    dflipflop s0 (.D(B[0]), .CKT(CKT), .Q(W[0]));  
    dflipflop s1 (.D(B[1]), .CKT(CKT), .Q(W[1]));  
    dflipflop s2 (.D(B[2]), .CKT(CKT), .Q(W[2]));
```

```

dfflipflop s3 (.D(B[3]), .CKT(CKT), .Q(W[3]));
dfflipflop s4 (.D(B[4]), .CKT(CKT), .Q(W[4]));
dfflipflop s5 (.D(B[5]), .CKT(CKT), .Q(W[5]));
dfflipflop s6 (.D(B[6]), .CKT(CKT), .Q(W[6]));
dfflipflop s7 (.D(B[7]), .CKT(CKT), .Q(W[7]));

```

```

PriorityEncoder p1(B,F);

```

```

endmodule

```

```

module BlockChooser_tb;

```

```

reg [7:0]B;
wire [2:0]F;

```

```

BlockChooser b1(B,F);

```

```

initial begin

```

```

    $dumpfile("BlockChooser.vcd");
    $dumpvars(0,BlockChooser_tb);

```

```

end

```

```

initial begin

```

```

    $display("|B0 |B1 |B2 |B3 |B4 |B5 |B6 |B7 | BlockNumber |");
    $monitor("| %b | %b | %b | %b | %b | %b | %b | %b |    %b
|",B[0],B[1],B[2],B[3],B[4],B[5],B[6],B[7],F);

```

```

    //Let B and be something intially
    B=8'b10000000;

```

```

    //let Button 5 be pressed now
    #110 B=8'b00100000;
    //button is released now

```

```

    //For a while no button is pressed
    //But still, path to block 5 is shown

```

```

    //When car is parked, button 7 will get activated
    //Can be understood from logisim code
    //When car is entering, only 1 out of the 21 sensors(clocks) is 1 (odd parity, so xor
gives 1 as output)
    //So the xor part will give output 1 which is button 7

```

```

//So button 7 is pressed technically
//Once the car is parked
//That sensor(clock) will return 0
//So xor of all will become 0 again, as 0 sensors are 1 (0 is even parity, so xor gives 0
as output)
//So button is released again
//And path to block 7, empty path is shown
#170 B=8'b10000000;

//let Button 1 be pressed now
#210 B=8'b00000010;
//button is released now

//For a while no button is pressed
//But still, path to block 1 is shown

//When car is parked, button 7 will get activated
//Can be understood from logisim code
//When car is entering, only 1 out of the 21 sensors(clocks) is 1 (odd parity, so xor
gives 1 as output)
//So the xor part will give output 1 which is button 7
//So button 7 is pressed technically
//Once the car is parked
//That sensor(clock) will return 0
//So xor of all will become 0 again, as 0 sensors are 1 (0 is even parity, so xor gives 0
as output)
//So button is released again
//And path to block 7, empty path is shown
#270 B=8'b10000000;

end

initial #10000 $finish;

endmodule

```

## References

- Morris Mano, Digital Logic and Computer Design
- <https://www.flashparking.com/blog/what-is-an-automated-parkingsystem/>
- [www.wayleadr.com](http://www.wayleadr.com)
- <https://www.slideshare.net>
- Sunggu Lee, Advanced Digital Logic Design: Using VHDL, State Machines, and Synthesis for FPGAs

## Link to Resource Folder

[https://drive.google.com/drive/folders/1qaamQc11U\\_bVCfyj0aEIp9d-NobUFvID?usp=drive\\_link](https://drive.google.com/drive/folders/1qaamQc11U_bVCfyj0aEIp9d-NobUFvID?usp=drive_link)

The above link contains the Logisim Project (.circ files), Verilog codes (.v files), Screenshots of the circuits used